

**R. Ludwig and G. Bogdanov**  
**“RF Circuit Design: Theory and Applications”**  
**2<sup>nd</sup> edition**

**Figures for Chapter 2**

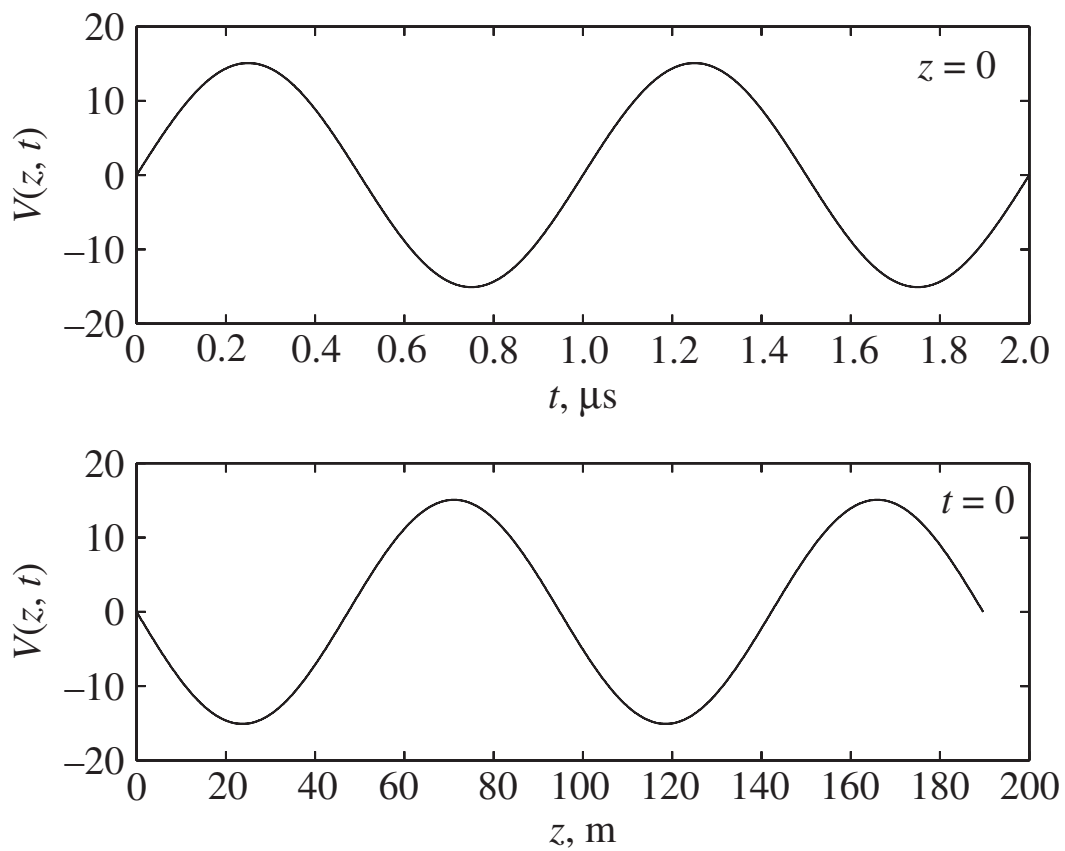


Figure 2-1 Voltage distribution as a function of time ( $z = 0$ ) and as a function of space ( $t = 0$ ).

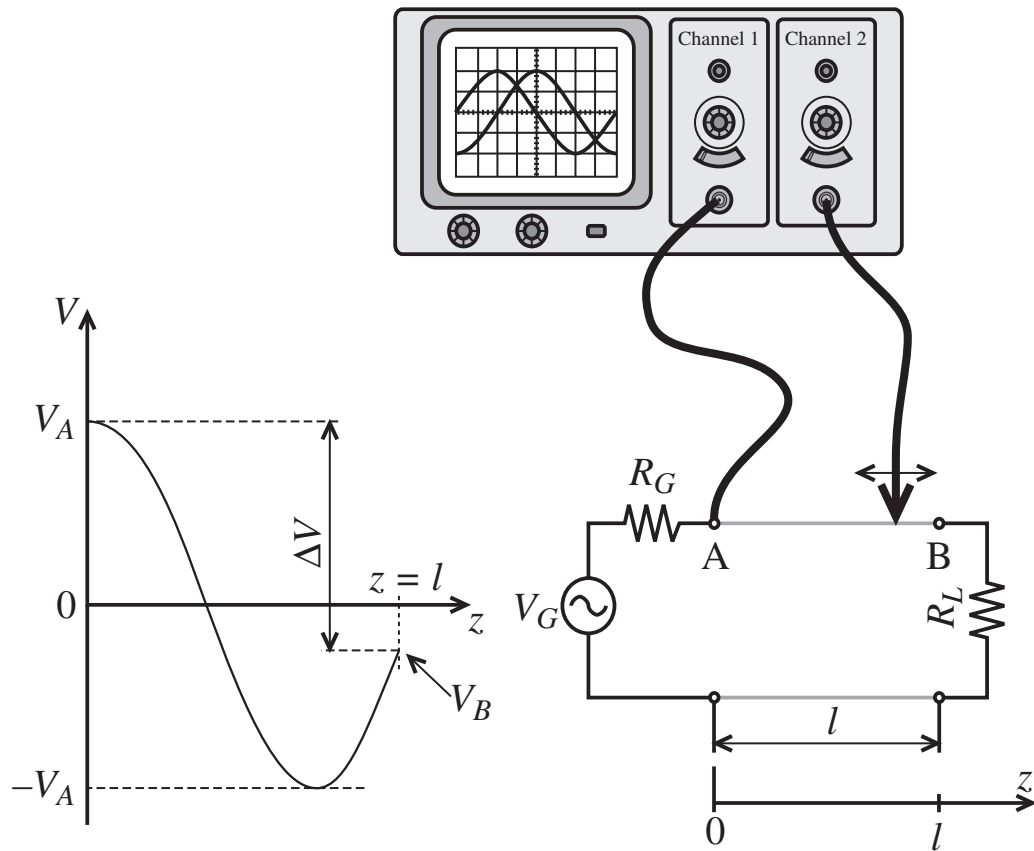


Figure 2-2 Amplitude measurements of 10 GHz voltage signal at the beginning (location A) and somewhere along a wire connecting load to source.

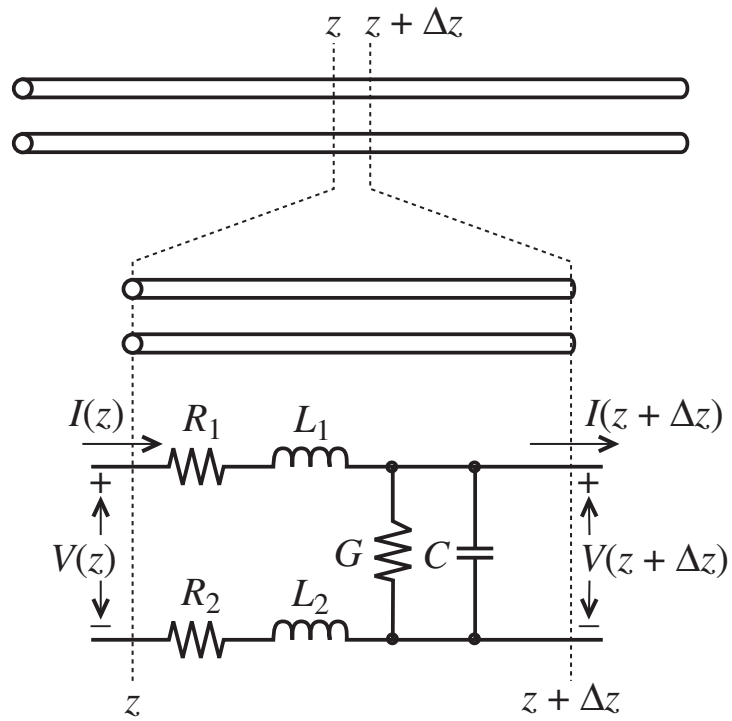


Figure 2-3 Partitioning an electric line into small elements  $\Delta z$  over which Kirchhoff's laws of constant voltage and current can be applied.

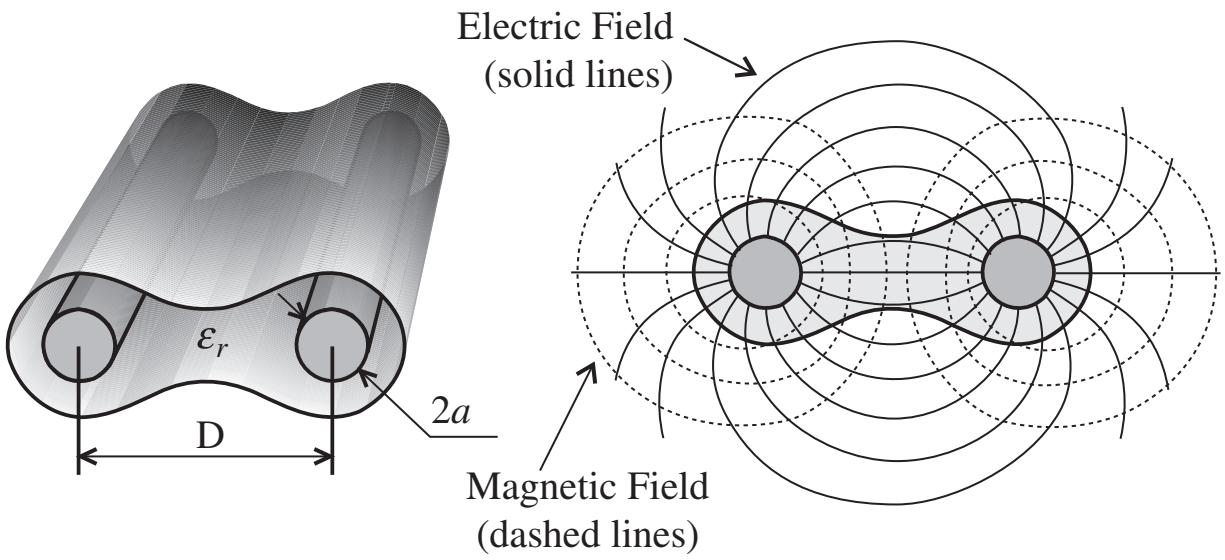


Figure 2-4 Geometry and field distribution in two-wire parallel conductor transmission line.



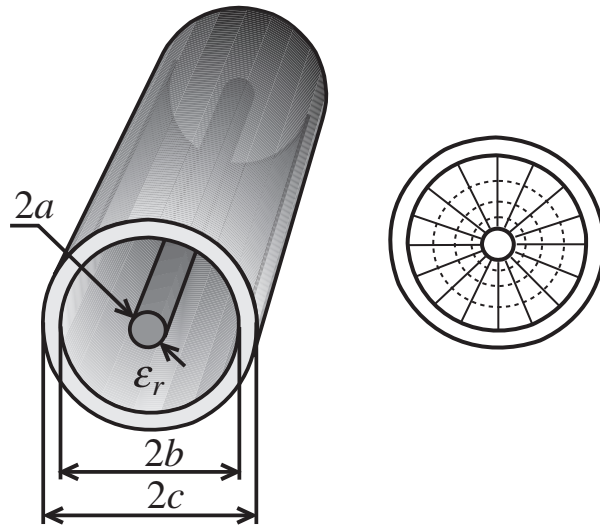


Figure 2-5 Coaxial cable transmission line.

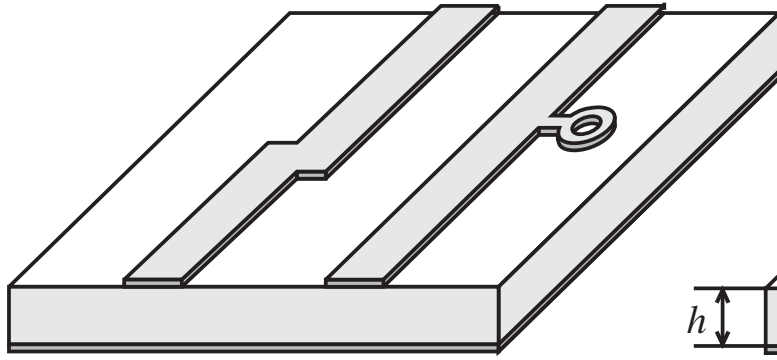


(a) Printed circuit board section

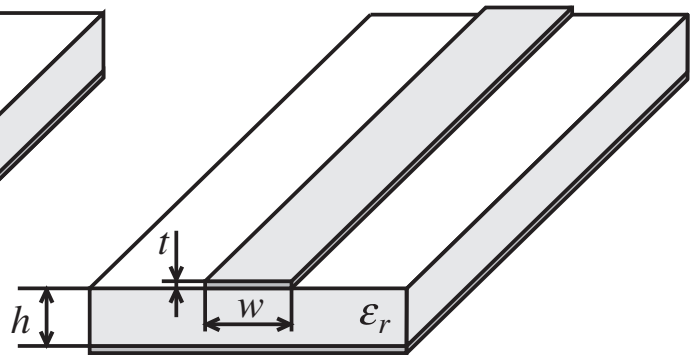


(b) Microstrip line

Figure 2-6 Microstrip transmission line representation.

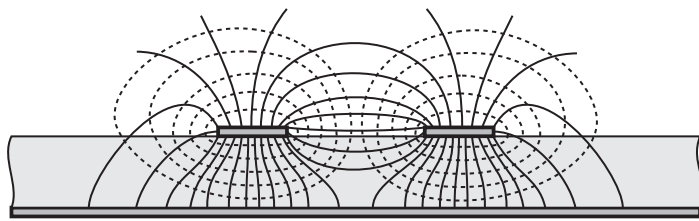


(a) Teflon epoxy ( $\epsilon_r = 2.55$ )

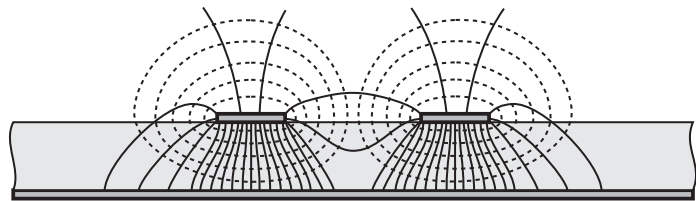


(b) Alumina ( $\epsilon_r = 10.0$ )

Figure 2-7 Electric flux density field leakage as a function of dielectric constants.

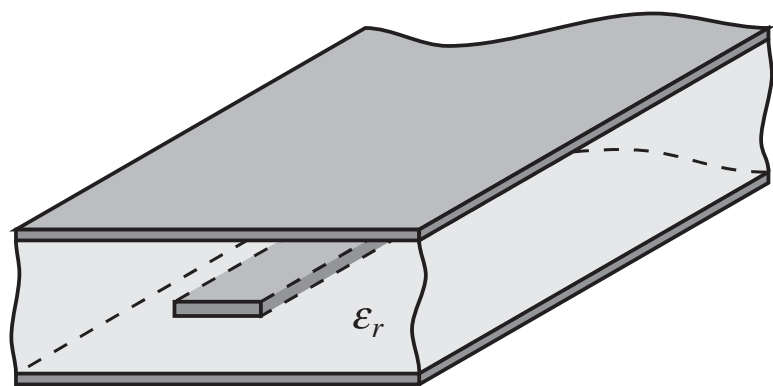


(a) Sandwich structure

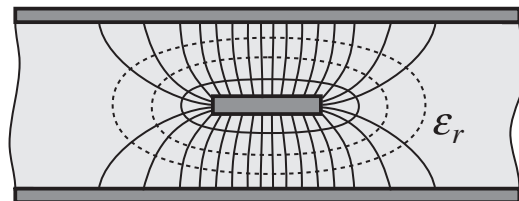


(b) Cross-sectional field distribution

Figure 2-8 Triple-layer transmission line configuration.



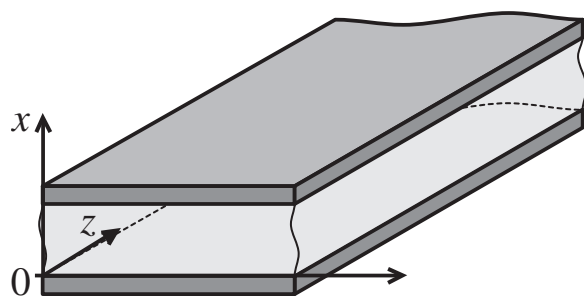

(a) Geometric representation

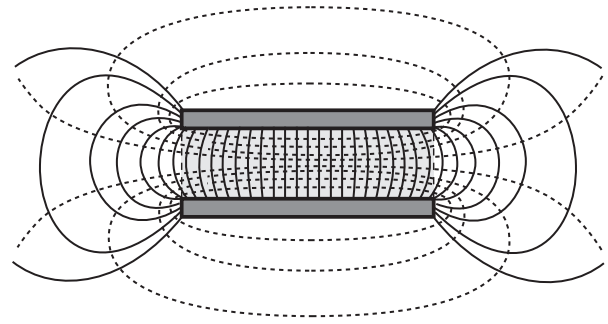

(b) Field distribution

Figure 2-9 Parallel-plate transmission line.

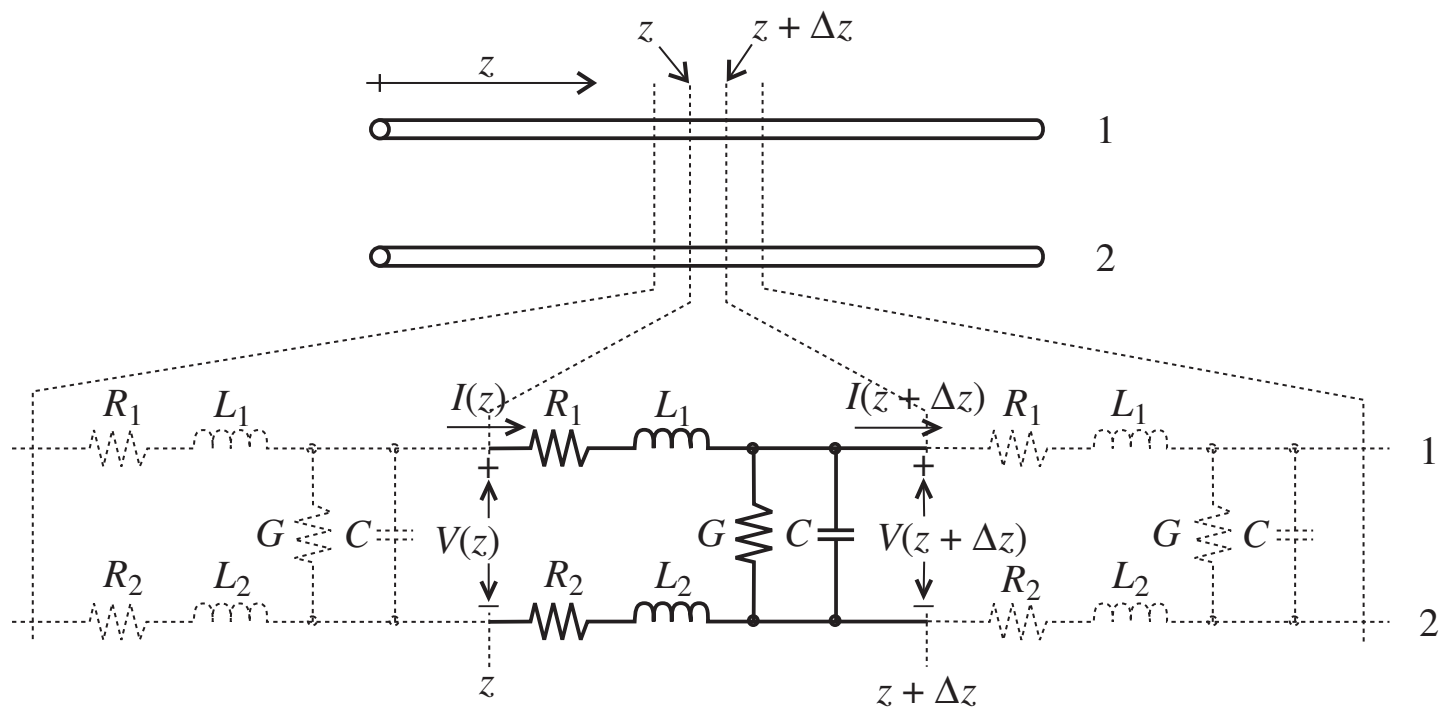


Figure 2-10 Segmentation of two-wire transmission line into  $\Delta z$ -long sections suitable for lumped parameter analysis.

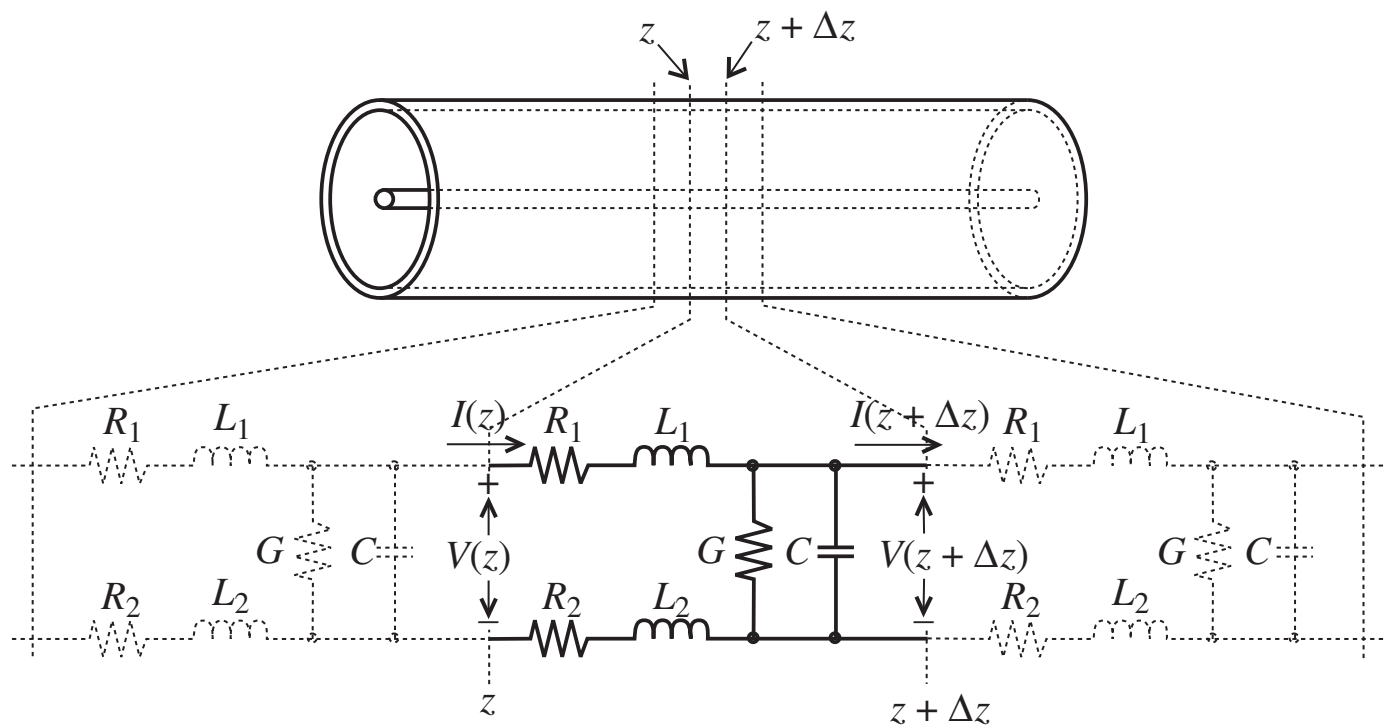


Figure 2-11 Segmentation of a coaxial cable into  $\Delta z$  length elements suitable for lumped parameter analysis.

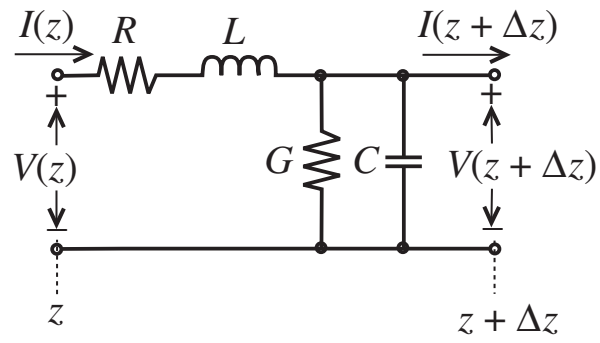


Figure 2-12 Generic electric equivalent circuit representation.

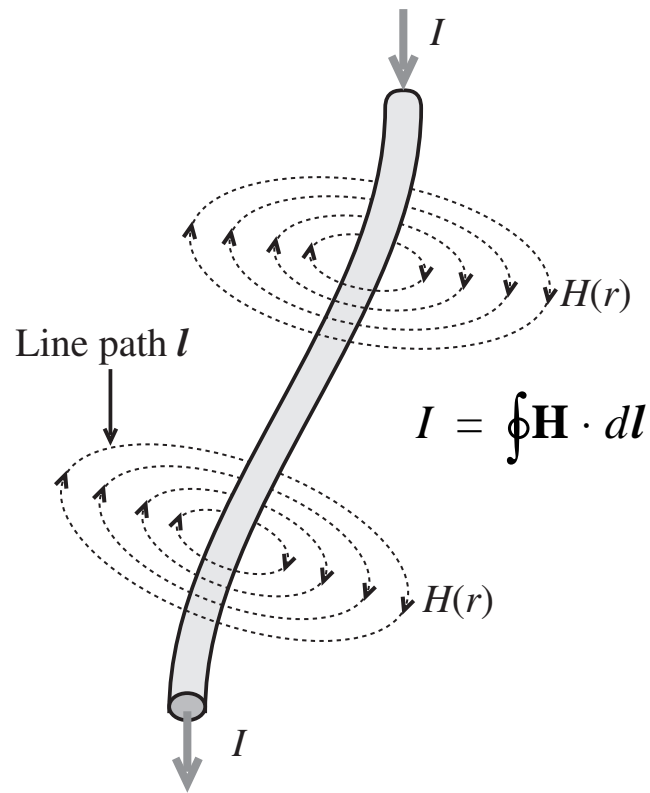


Figure 1-1 Ampère's law linking the current flow to the magnetic field.

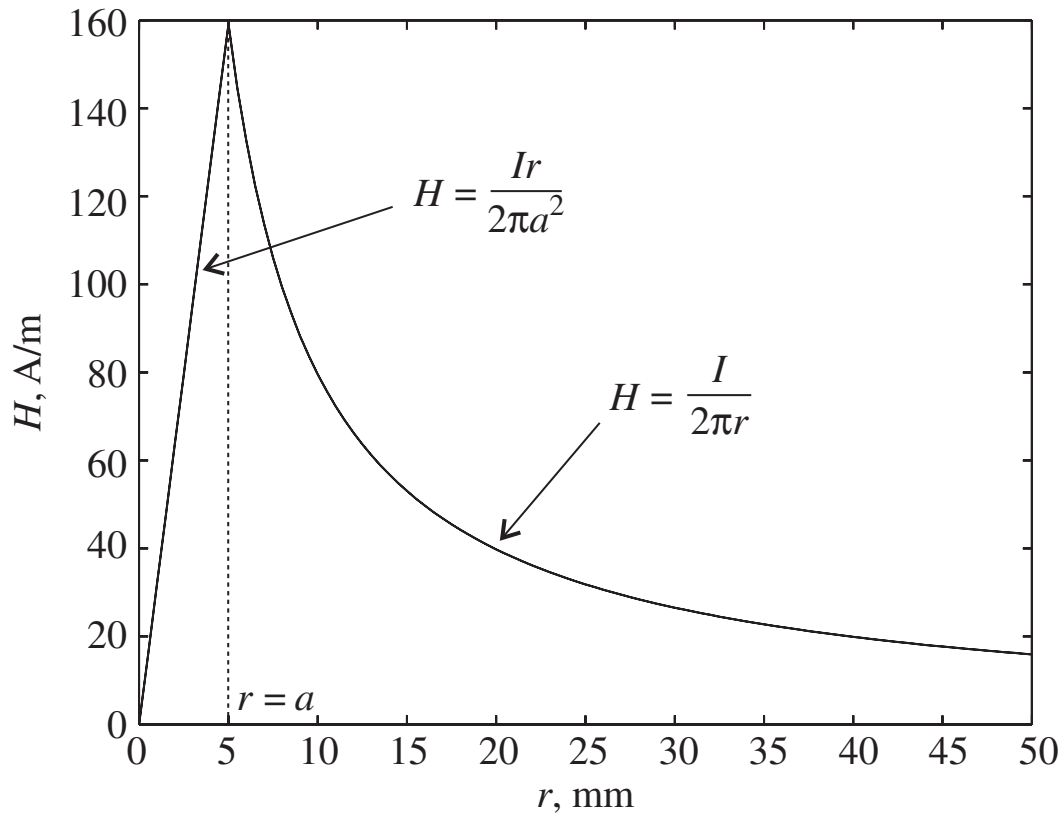


Figure 2-13 Magnetic field distribution inside and outside of an infinitely long wire of radius  $a = 5$  mm carrying a current of 5 A.

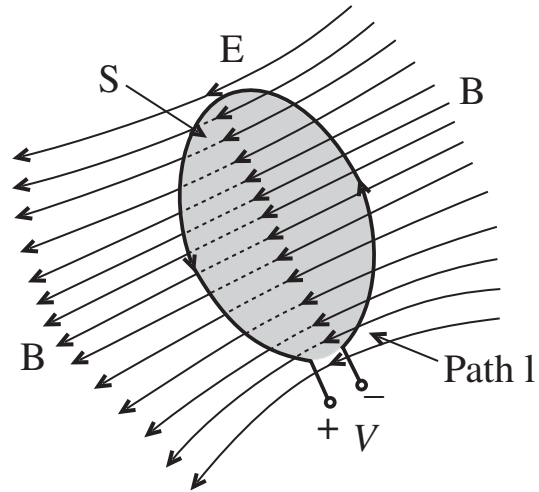


Figure 2-14 The time rate of change of the magnetic flux density induces a voltage.

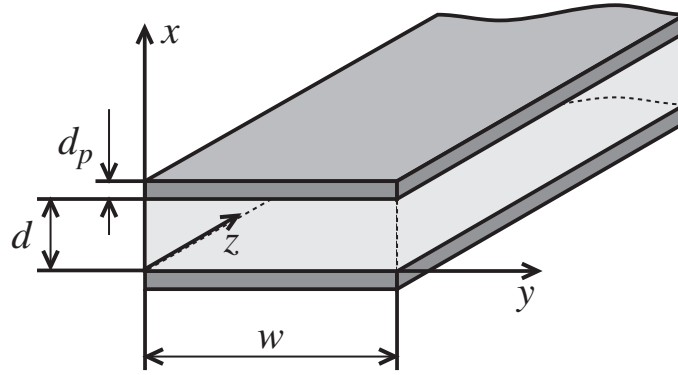


Figure 2-15 Parallel-plate transmission line geometry. The plate width  $w$  is large compared with the separation  $d$ .



Table 2-1 Transmission line parameters for three line types

Parameter	Two-Wire Line	Coaxial Line	Parallel-Plate Line
$R$ $\Omega/\text{m}$	$\frac{1}{\pi a \sigma_{\text{cond}} \delta}$	$\frac{1}{2\pi \sigma_{\text{cond}} \delta} \left( \frac{1}{a} + \frac{1}{b} \right)$	$\frac{2}{w \sigma_{\text{cond}} \delta}$
$L$ $\text{H/m}$	$\frac{\mu}{\pi} \cosh^{-1} \left( \frac{D}{2a} \right)$	$\frac{\mu}{2\pi} \ln \left( \frac{b}{a} \right)$	$\mu \frac{d}{w}$
$G$ $\text{S/m}$	$\frac{\pi \sigma_{\text{diel}}}{\cosh^{-1} (D/(2a))}$	$\frac{2\pi \sigma_{\text{diel}}}{\ln (b/a)}$	$\sigma_{\text{diel}} \frac{w}{d}$
$C$ $\text{F/m}$	$\frac{\pi \epsilon}{\cosh^{-1} (D/(2a))}$	$\frac{2\pi \epsilon}{\ln (b/a)}$	$\epsilon \frac{w}{d}$

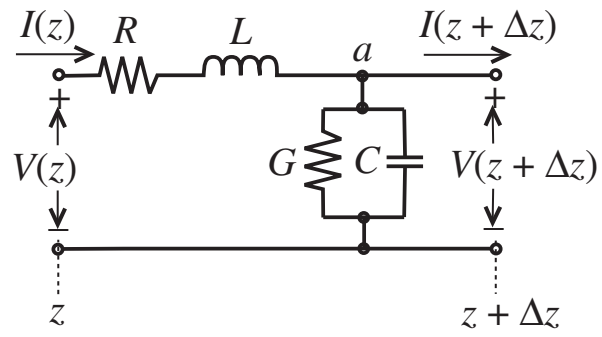


Figure 2-16 Segment of a transmission line with voltage loop and current node.

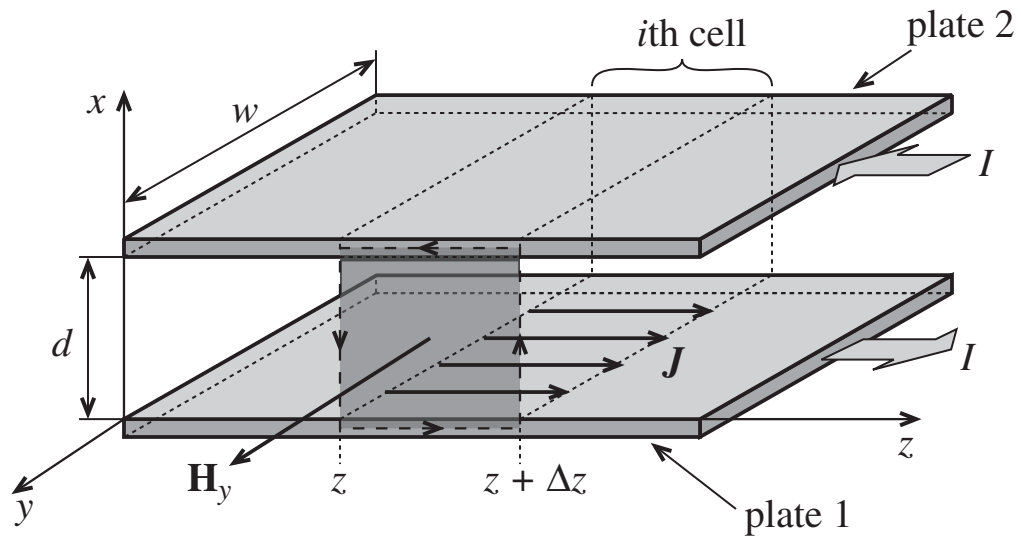


Figure 2-17 Integration surface element for Faraday's law application.

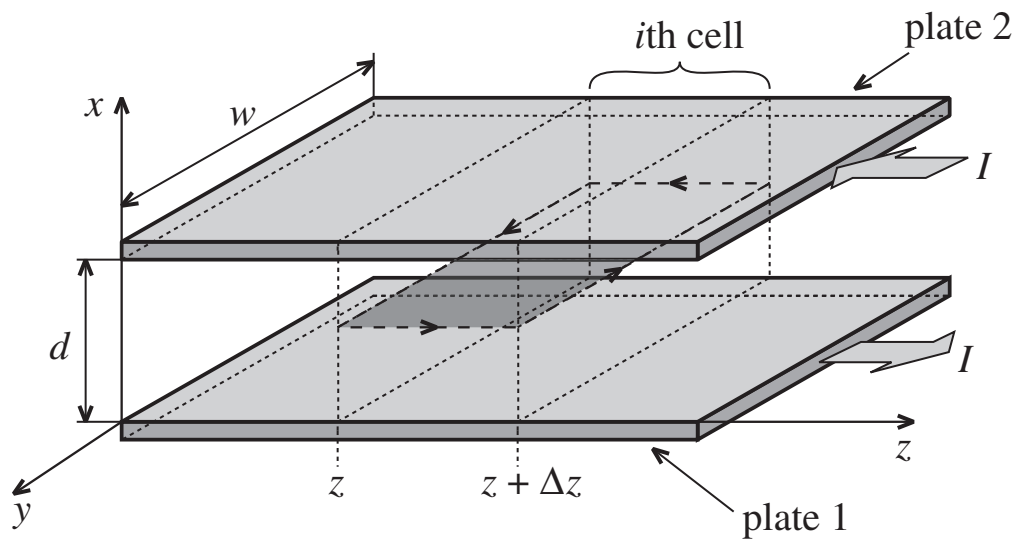


Figure 2-18 Surface element used to apply Ampère's law.

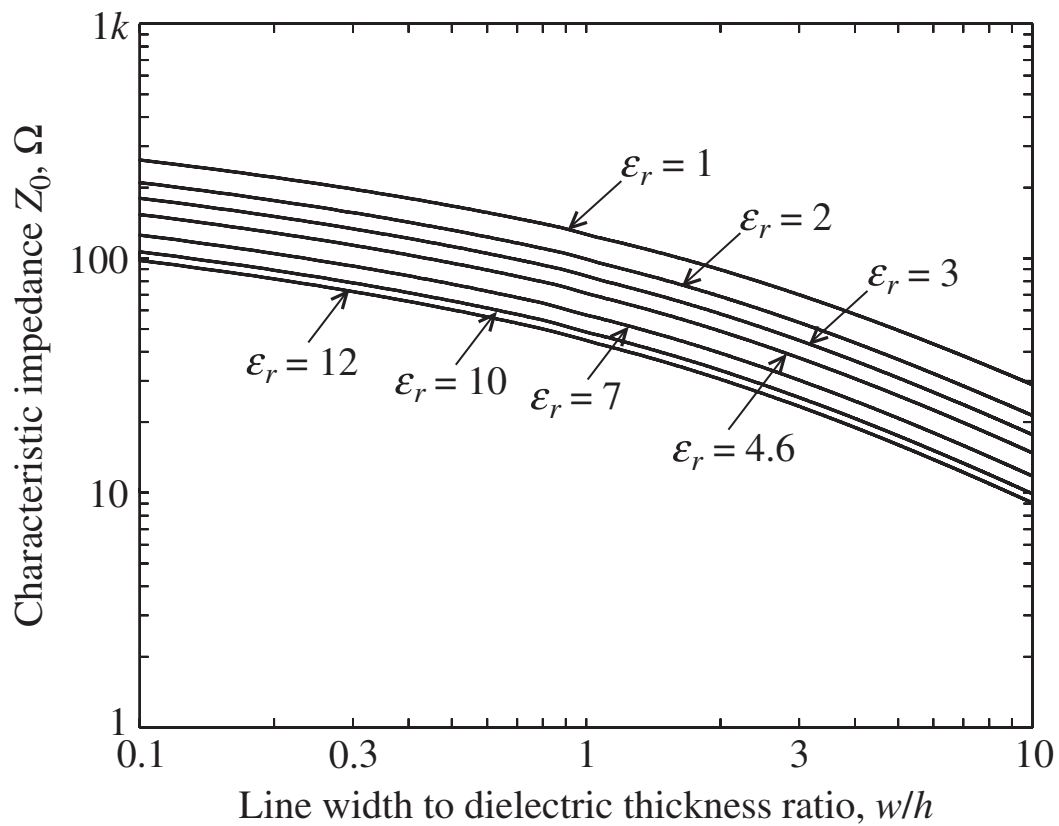


Figure 2-19 Microstrip characteristic impedance as a function of  $w/h$ .

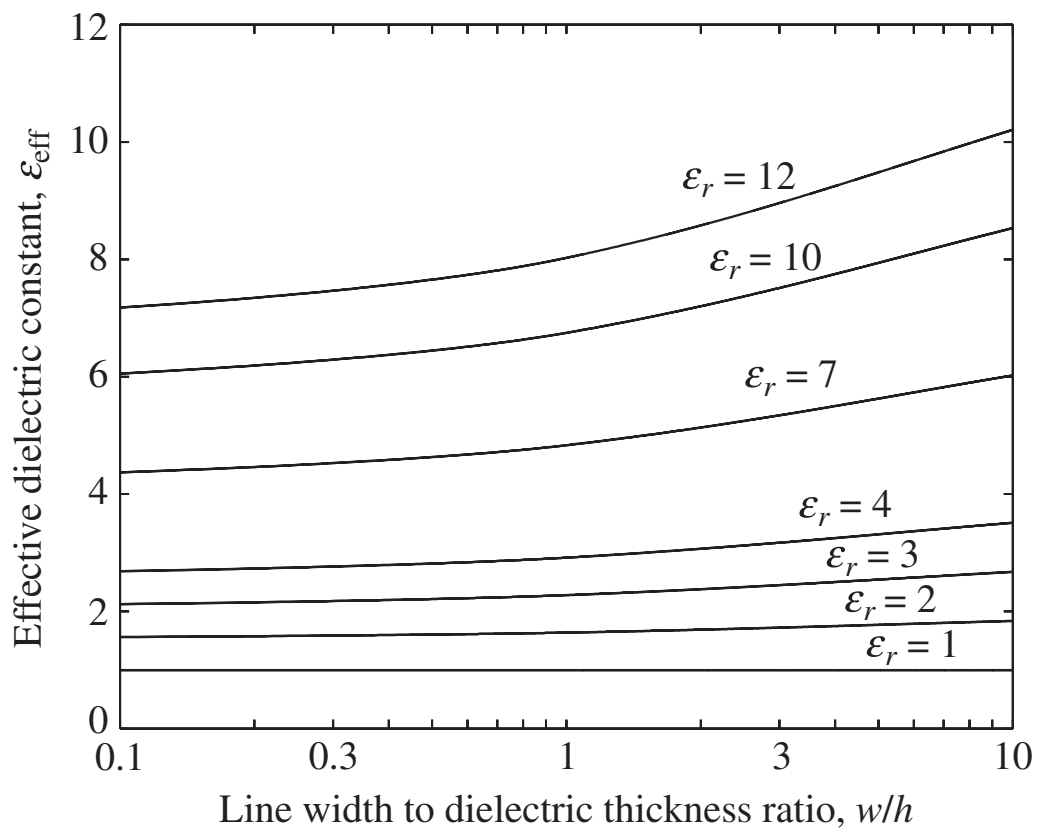


Figure 2-20 Effective dielectric constant of the microstrip line as a function of  $w/h$  for different dielectric constants.

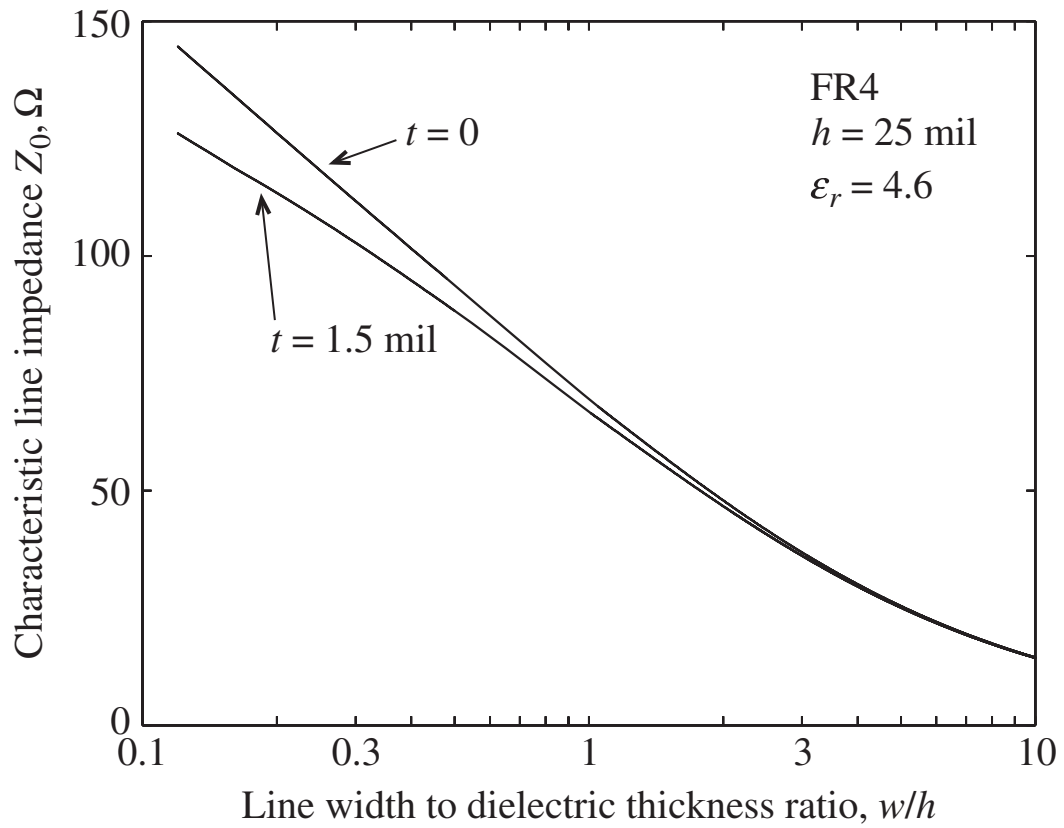


Figure 2-21 Effect of conductor thickness on the characteristic impedance of a microstrip line placed on a 25 mil thick FR4 printed circuit board.

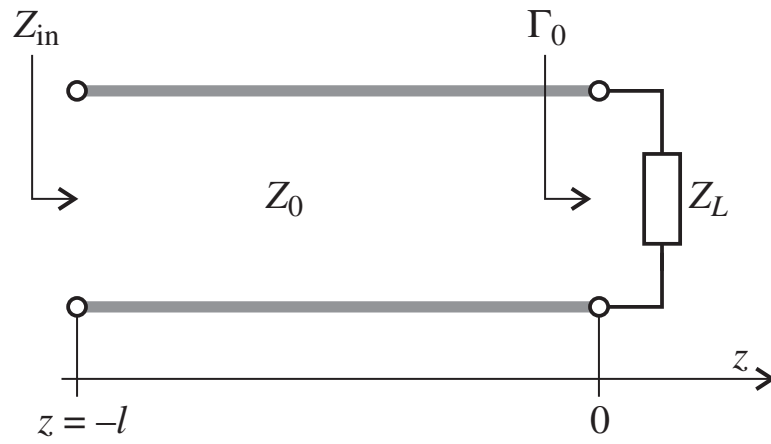


Figure 2-22 Terminated transmission line at location  $z = 0$ .



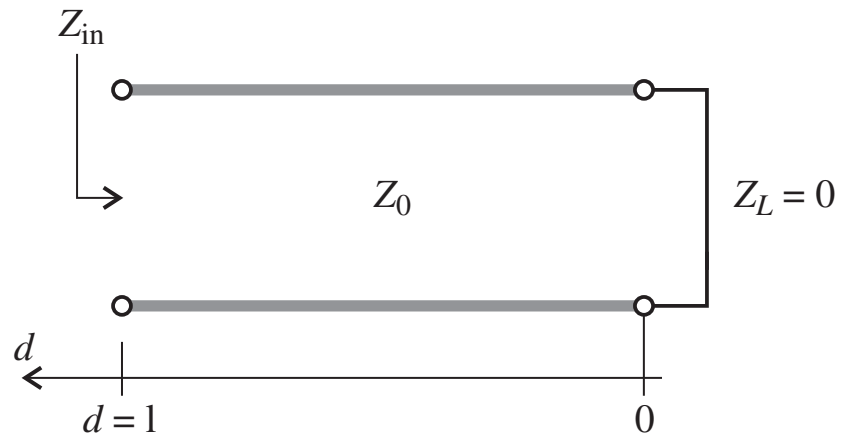


Figure 2-23 Short-circuited transmission line and new coordinate system  $d$ .

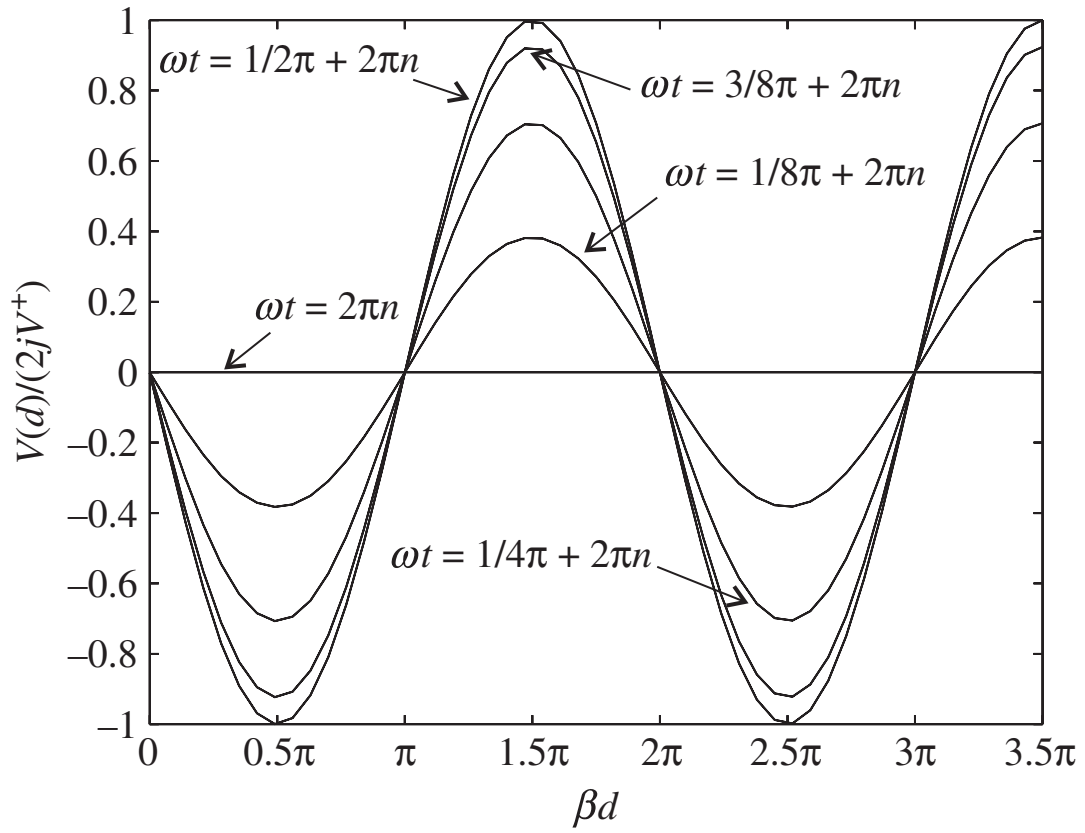


Figure 2-24 Standing wave pattern for various instances of time.

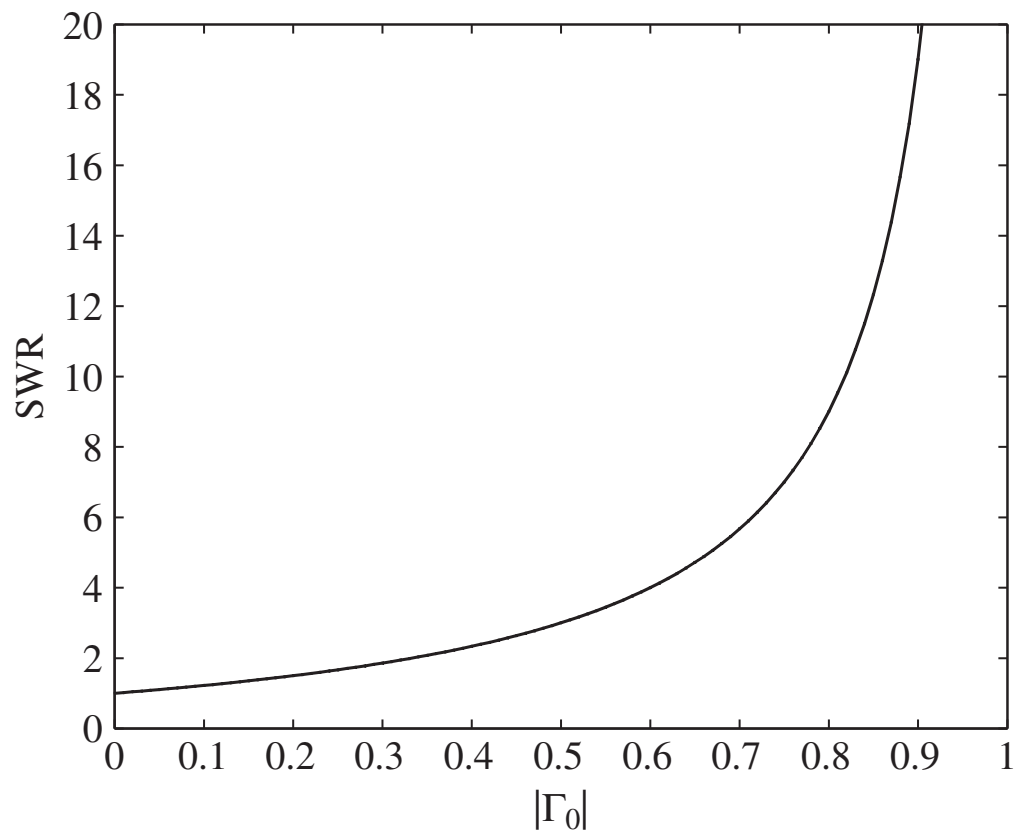


Figure 2-25 SWR as a function of load reflection coefficient  $|\Gamma_0|$ .

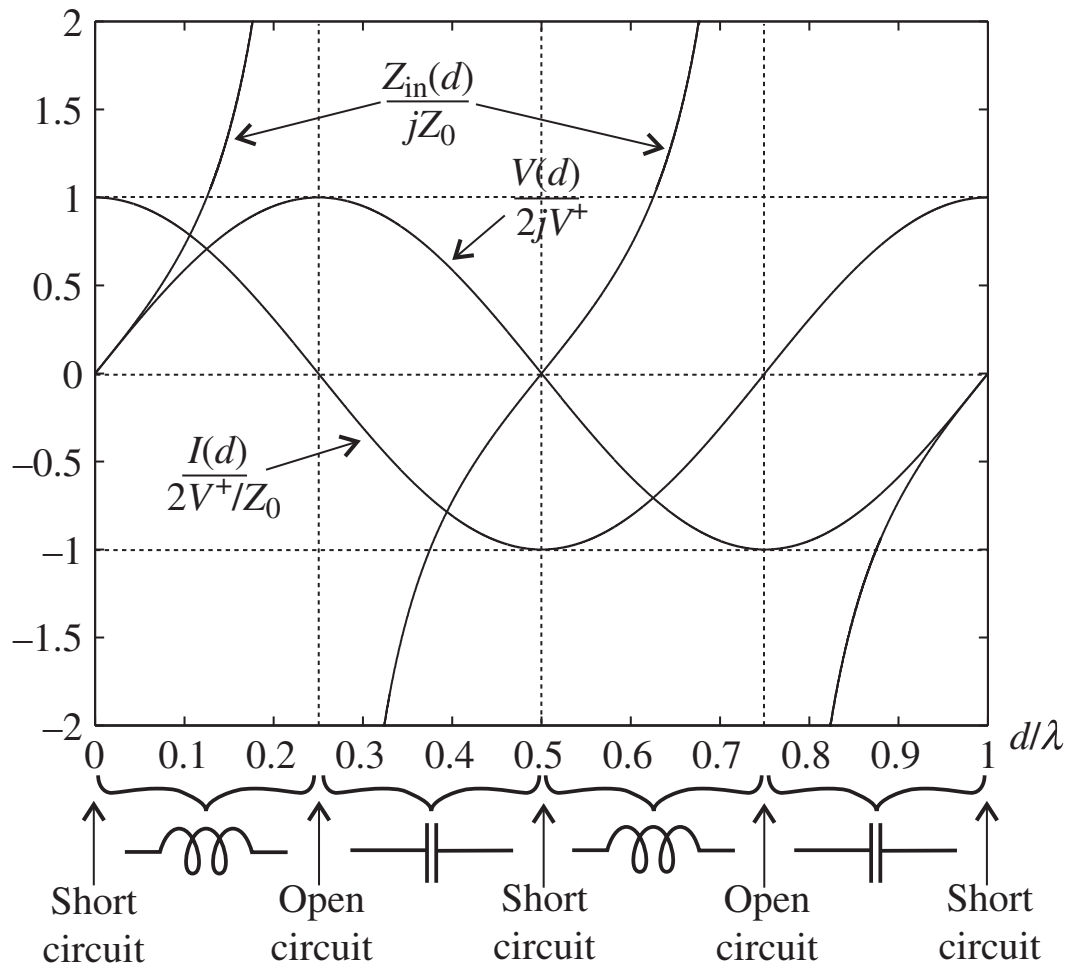


Figure 2-26 Voltage, current, and impedance as a function of line length for a short-circuit termination.

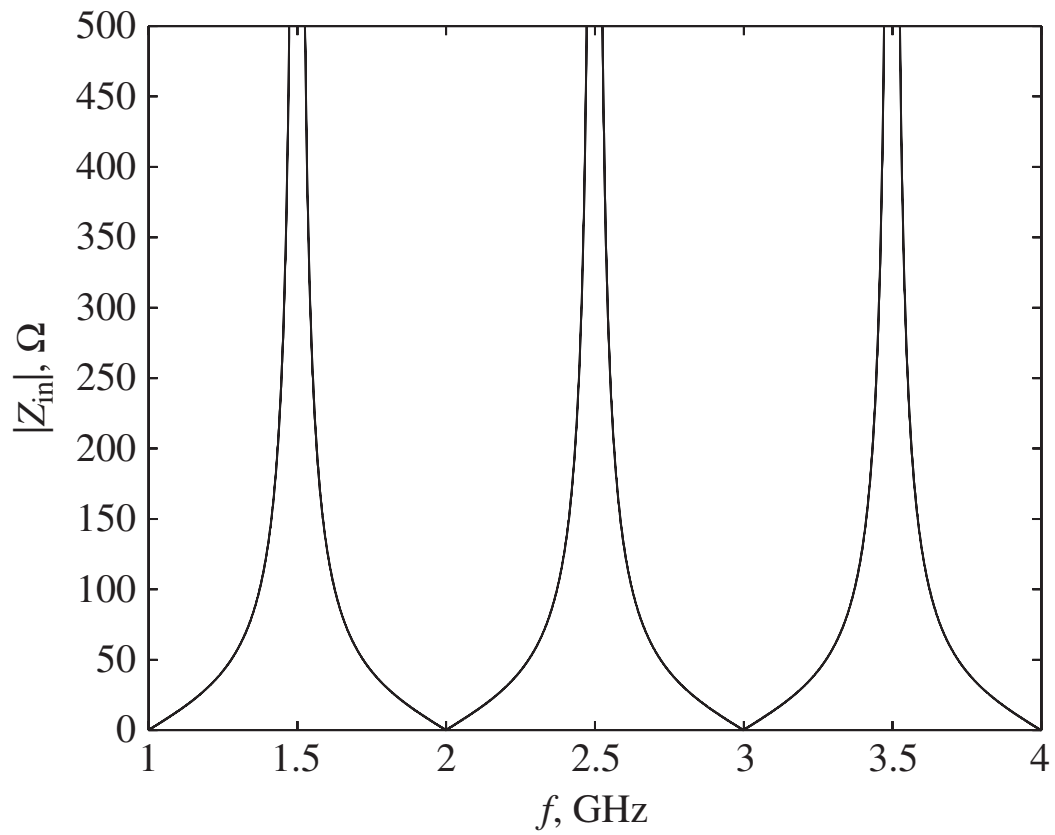


Figure 2-27 Magnitude of the input impedance for a 10 cm long, short-circuited transmission line as a function of frequency.

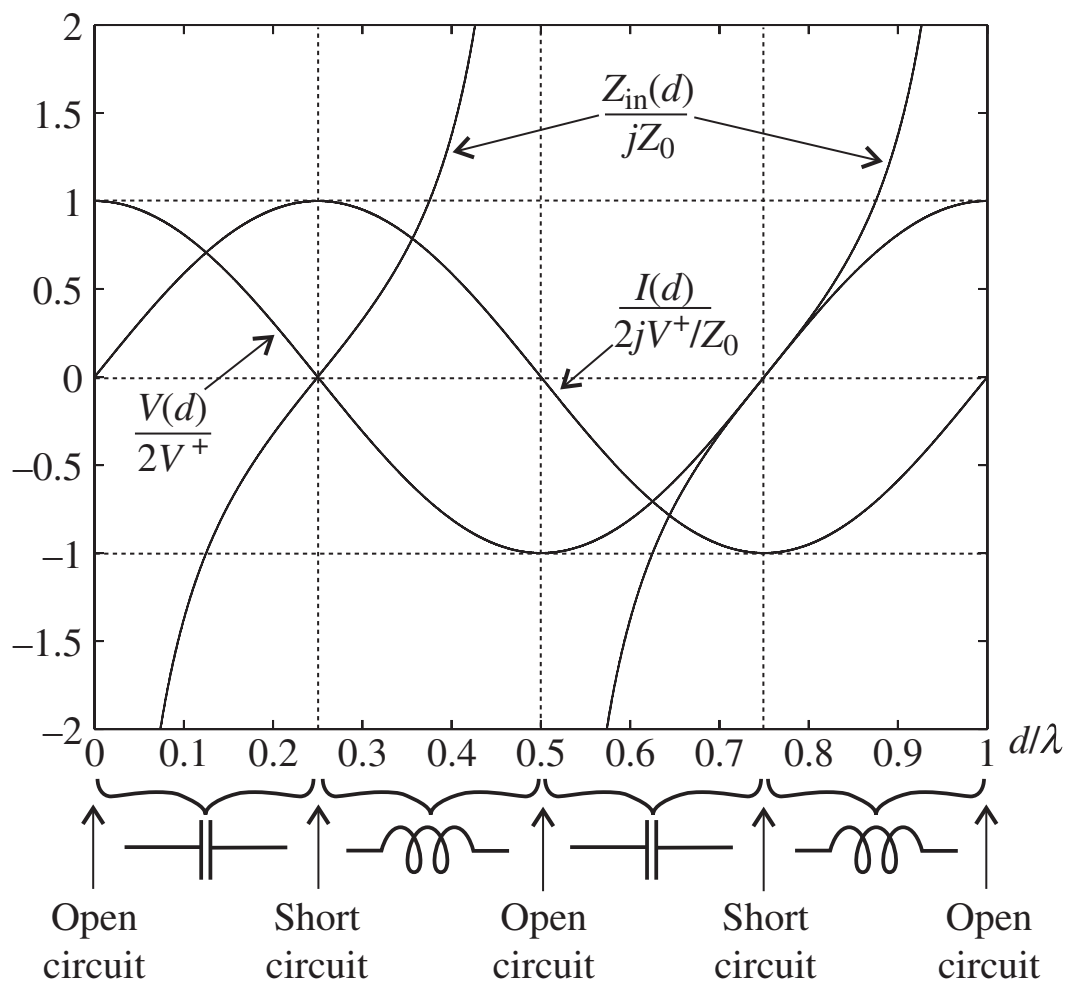


Figure 2-28 Voltage, current, and impedance as a function of line length for an open-circuit termination.

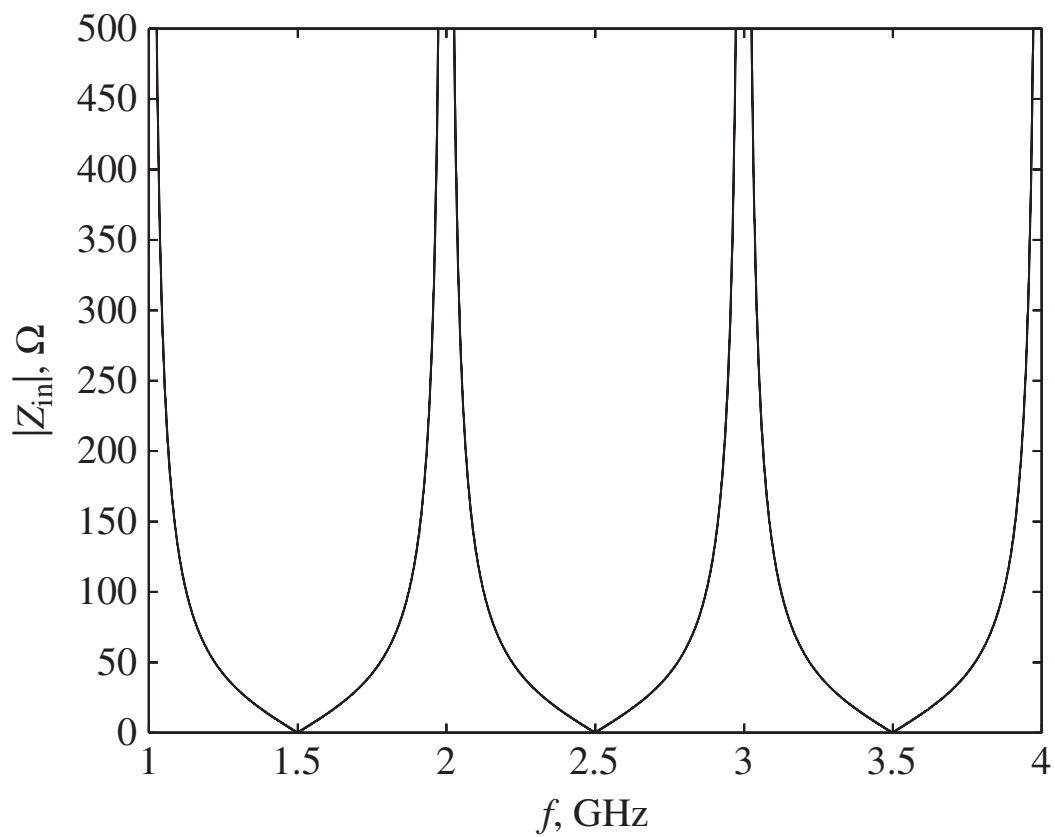


Figure 2-29 Impedance magnitude for a 10 cm long, open-circuited transmission line as a function of frequency.

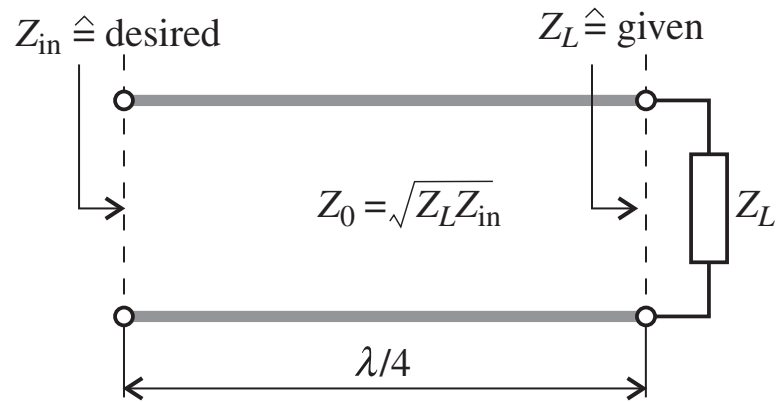


Figure 2-30 Input impedance matched to a load impedance through a  $\lambda/4$  line segment.



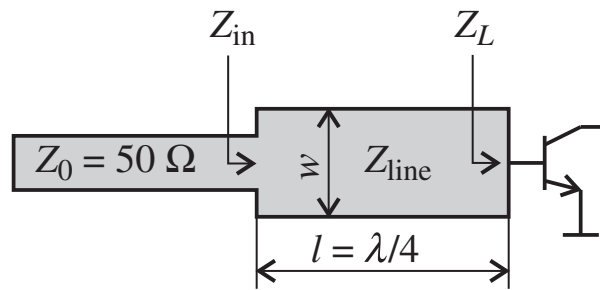


Figure 2-31 Input impedance of quarter-wave transformer.

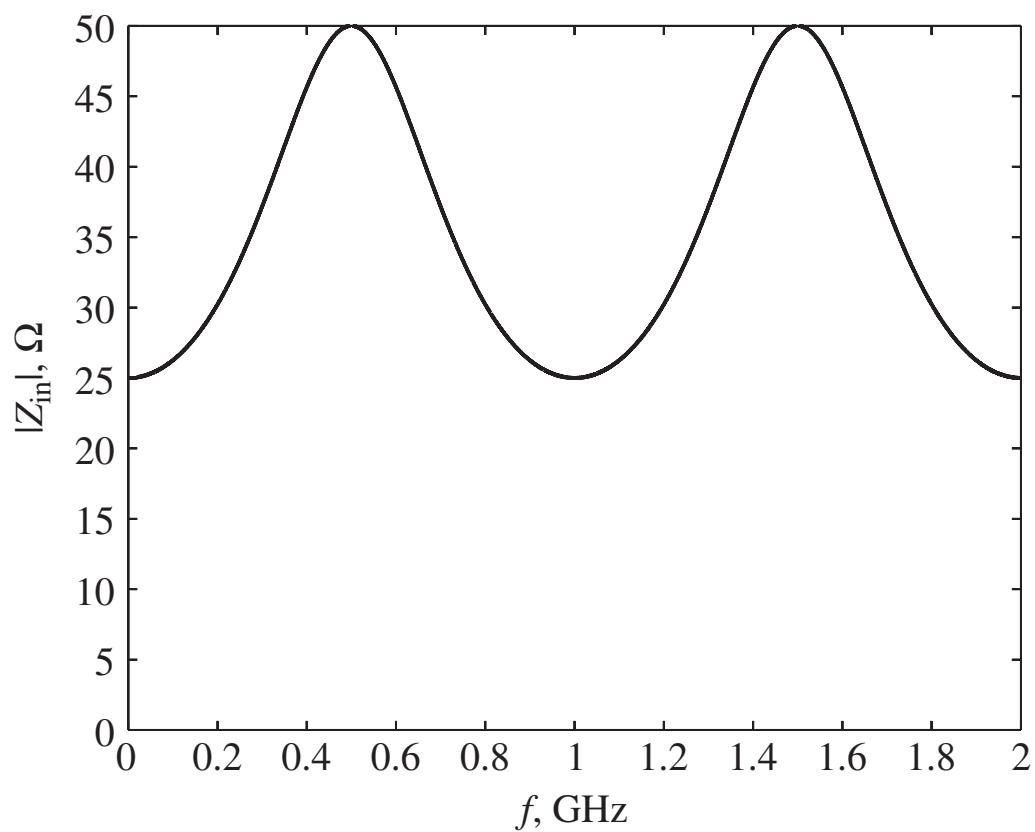


Figure 2-32 Magnitude of  $Z_{in}$  for frequency range of 0 to 2 GHz and fixed length  $d$ .

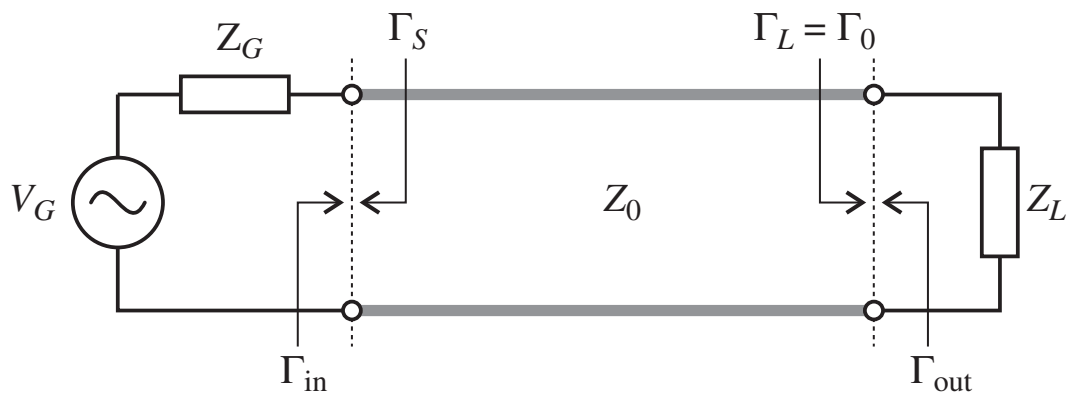


Figure 2-33 Generic transmission line circuit involving source and load terminations.



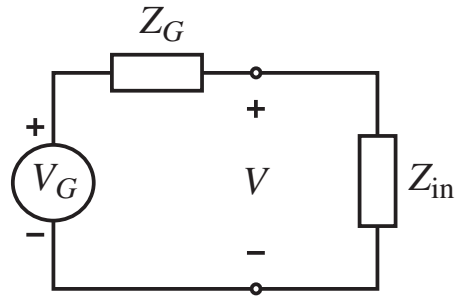


Figure 2-34    Equivalent lumped input network for a transmission line configuration.

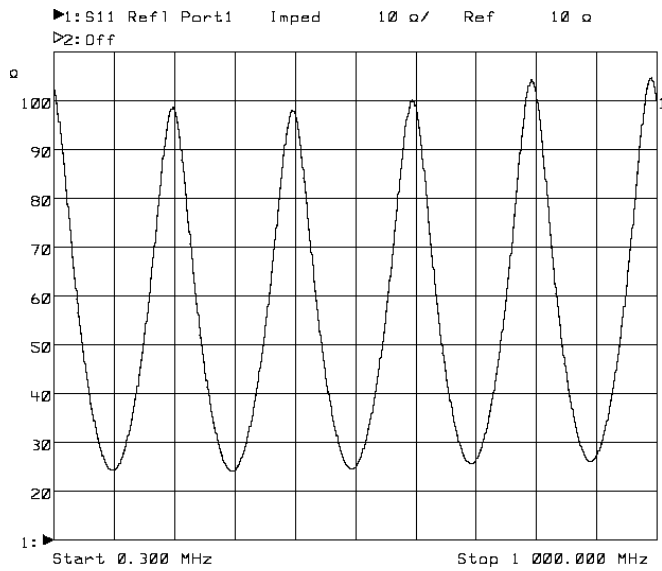

(a)

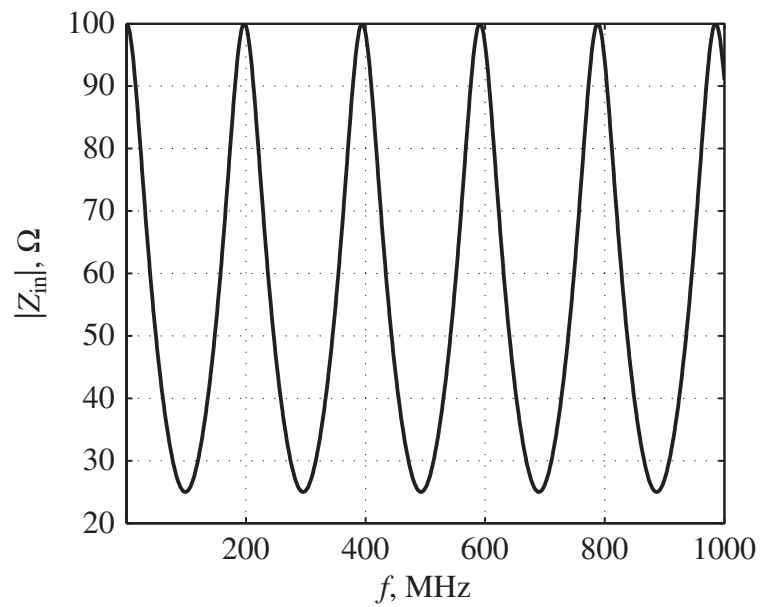

(b)

Figure 2-35 Impedance of a coaxial cable terminated by a 100  $\Omega$  resistor:  
 (a) network analyzer measurement, (b) theoretical prediction.

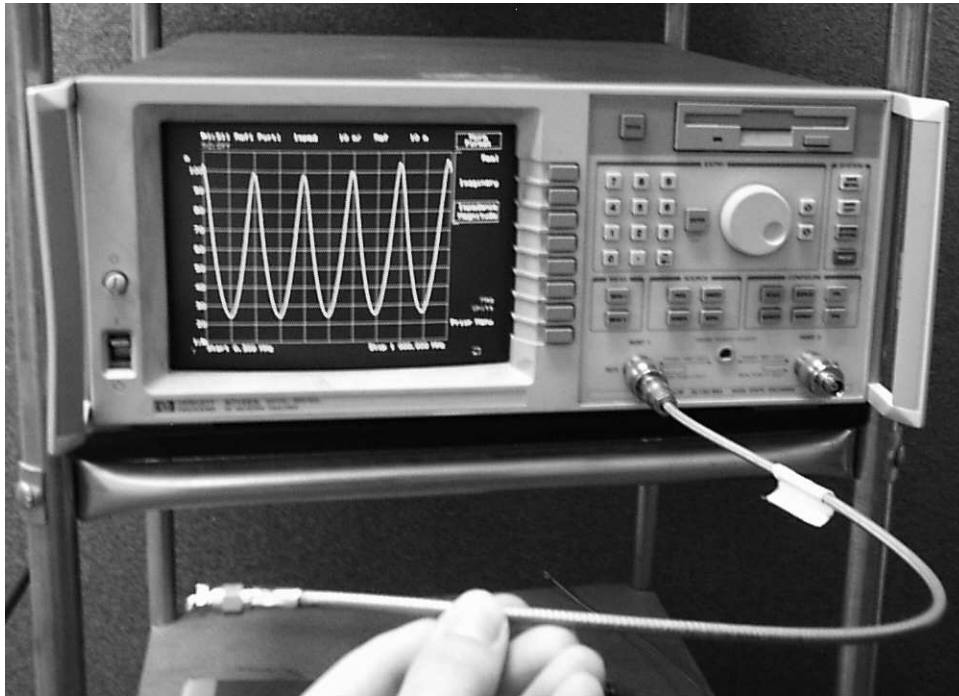


Figure 2-36 Network analyzer with the resistive  $100\ \Omega$  test load attached.