

R. Ludwig and G. Bogdanov
“RF Circuit Design: Theory and Applications”
2nd edition

Figures for Chapter 9



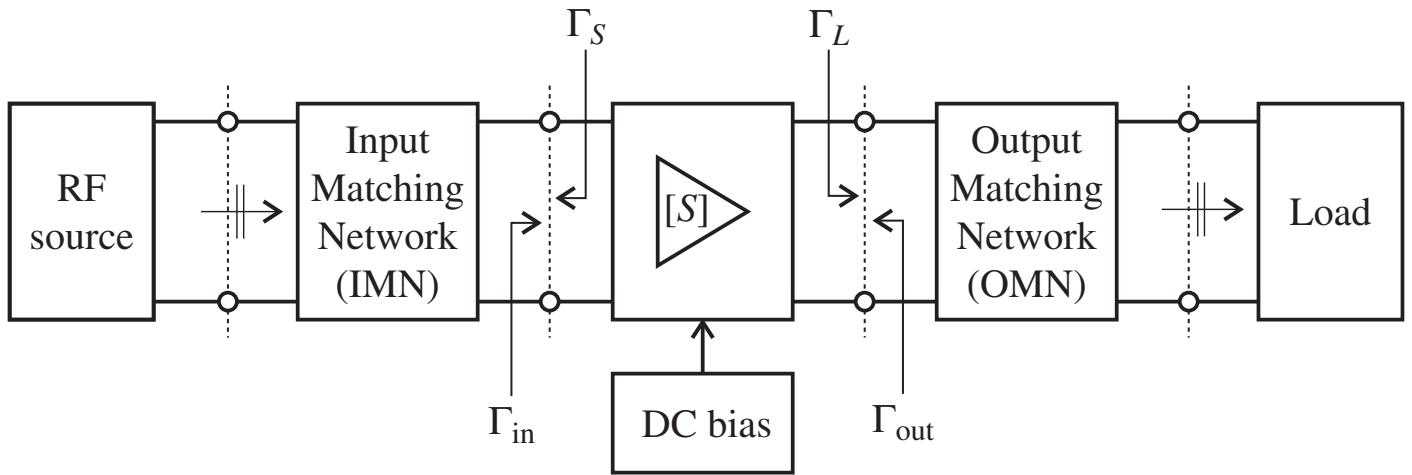


Figure 9-1 Generic amplifier system.

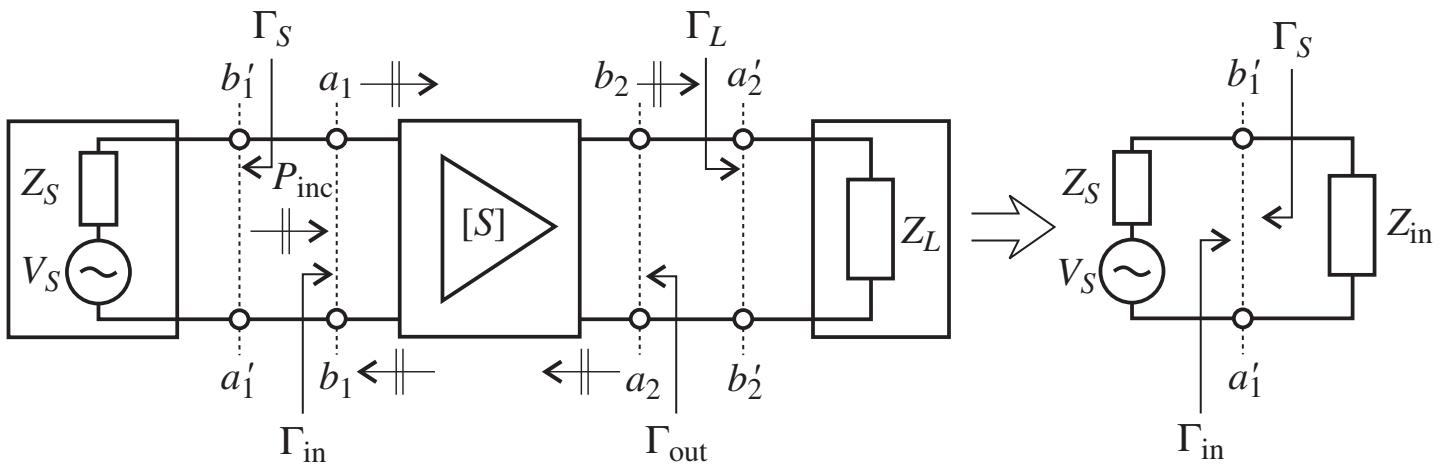


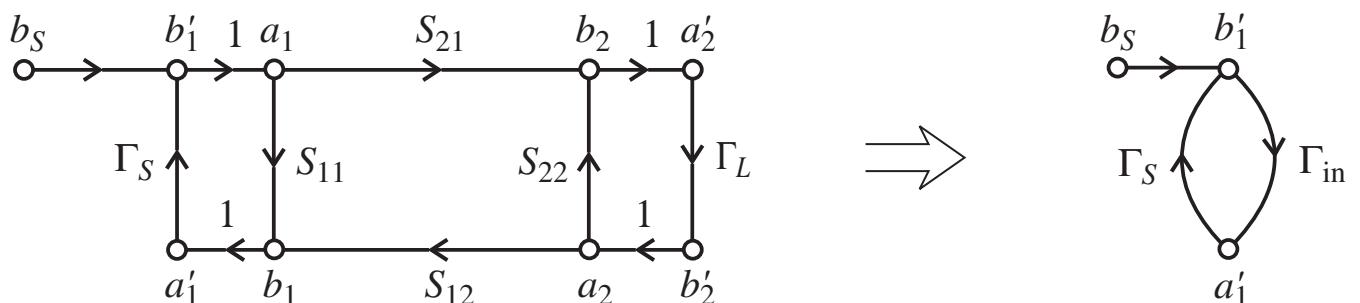(a) Simplified schematics of a single-stage amplifier




(b) Signal flow graph

Figure 9-2 Source and load connected to a single-stage amplifier network.

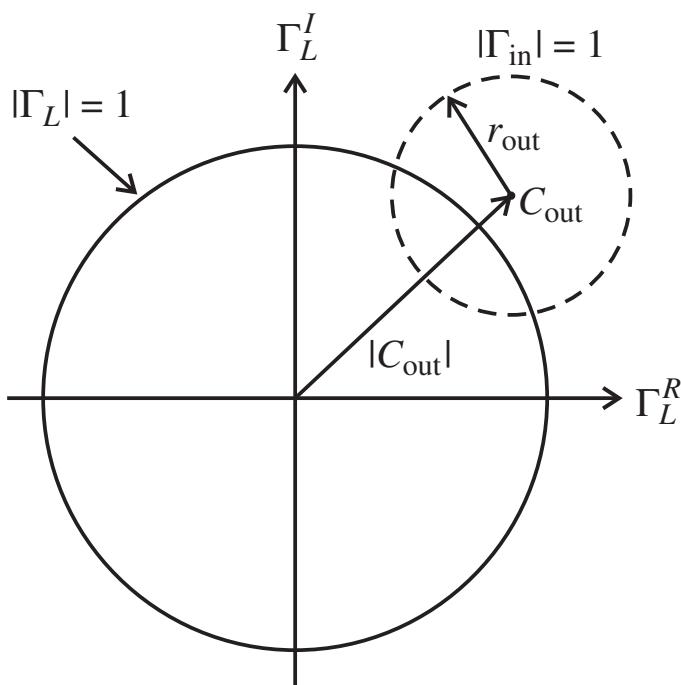


(a) Output stability circle

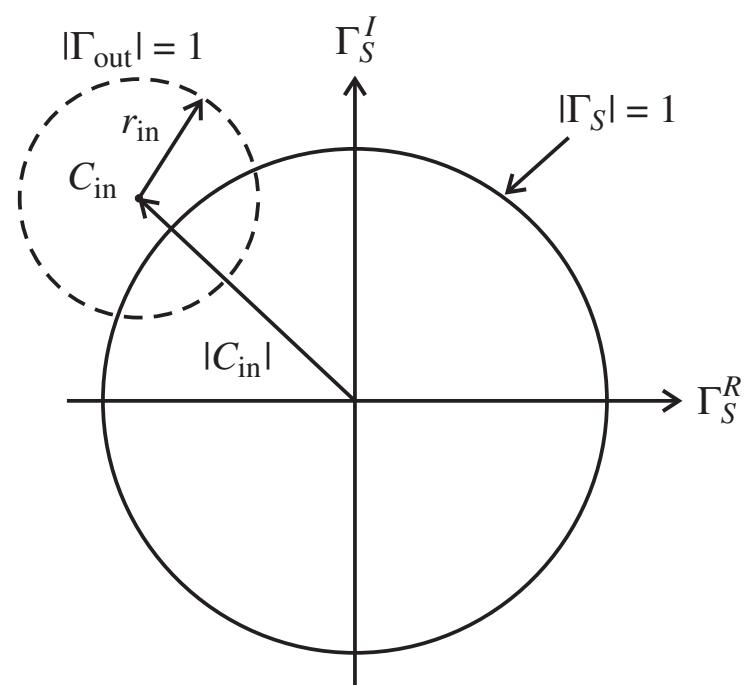


(b) Input stability circle

Figure 9-3 Stability circle $|\Gamma_{\text{in}}| = 1$ in the complex Γ_L -plane and stability circle $|\Gamma_{\text{out}}| = 1$ in the complex Γ_S -plane.

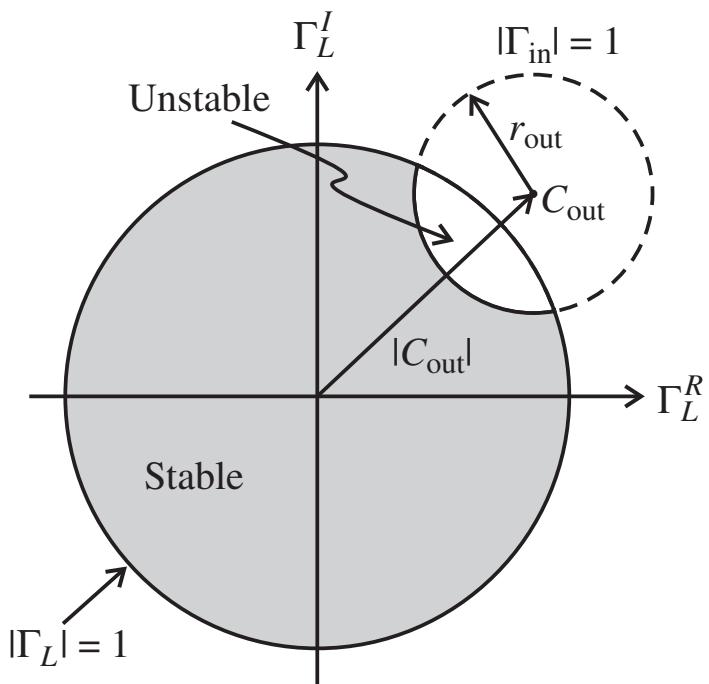


(a) Shaded region is stable,
since $|S_{11}| < 1$

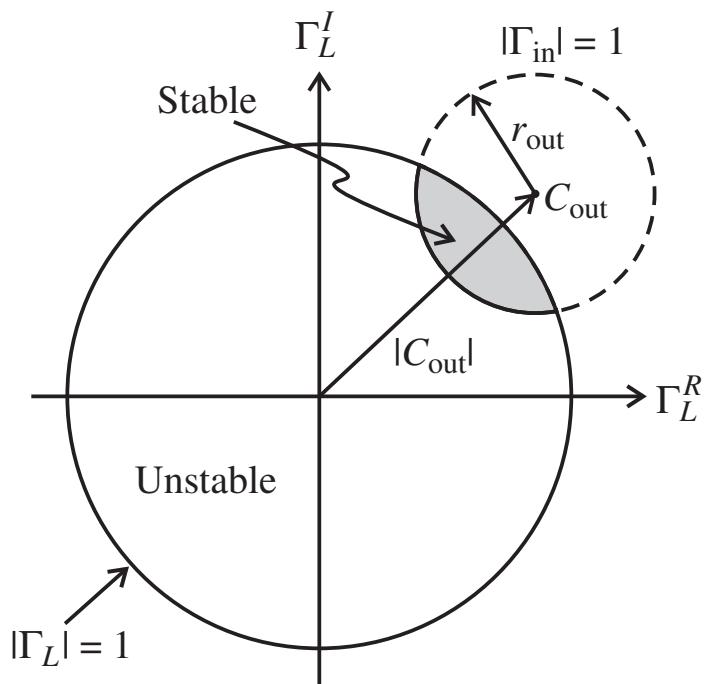


(a) Stable region excludes the origin,
 $\Gamma_L = 0$, since $|S_{11}| > 1$

Figure 9-4 Output stability circles denoting stable and unstable regions.

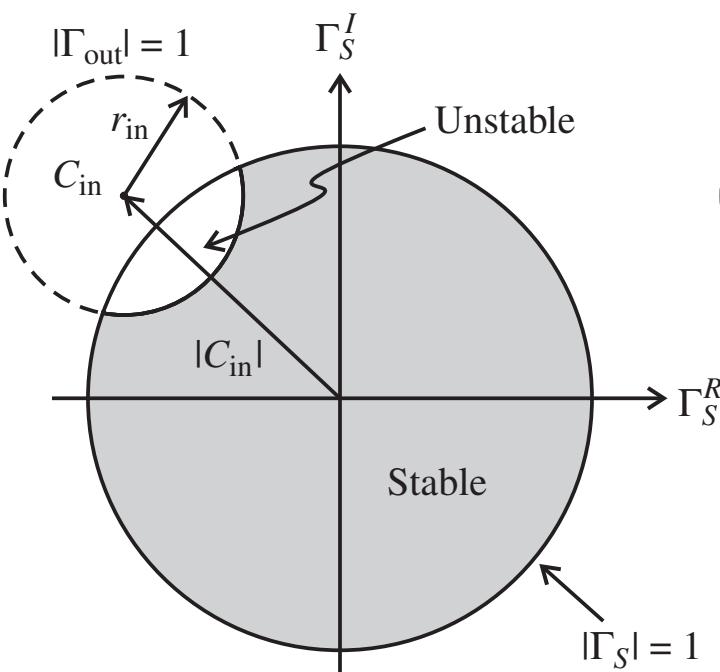

(a) $|S_{22}| < 1$

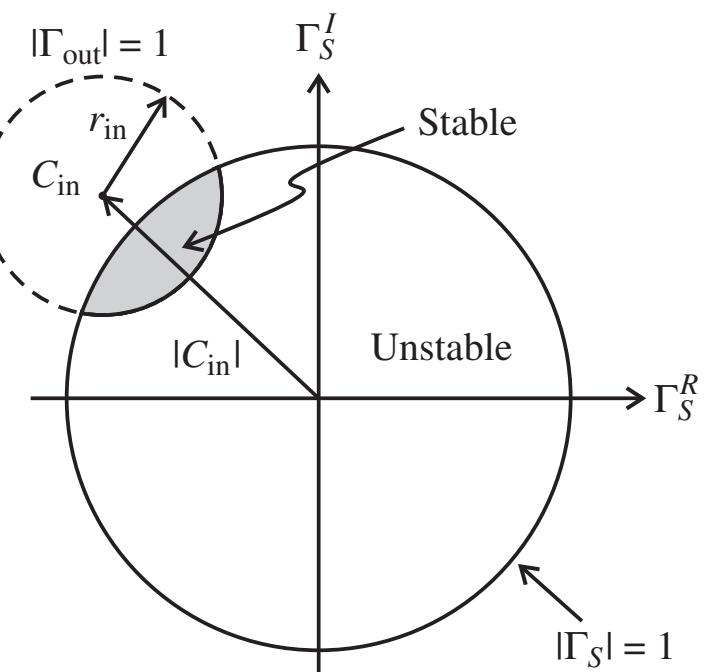

(b) $|S_{22}| > 1$

Figure 9-5 Input stability circles denoting stable and unstable regions.



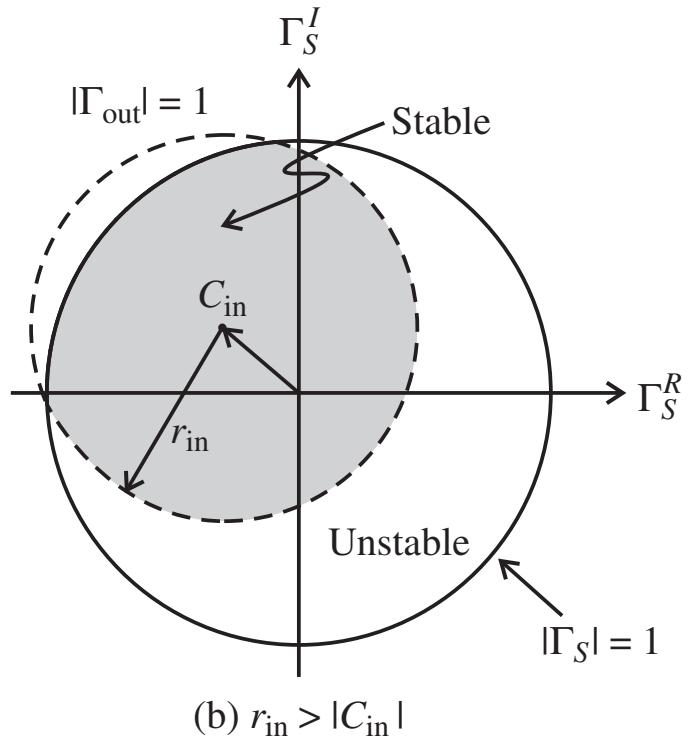
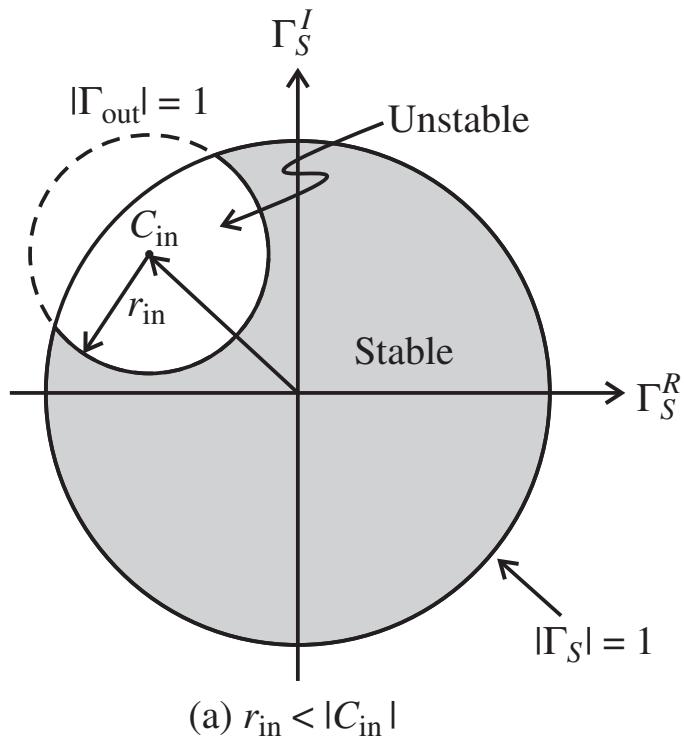


Figure 9-6 Different input stability regions for $|S_{22}| < 1$ depending on ratio between r_S and $|C_{\text{in}}|$.

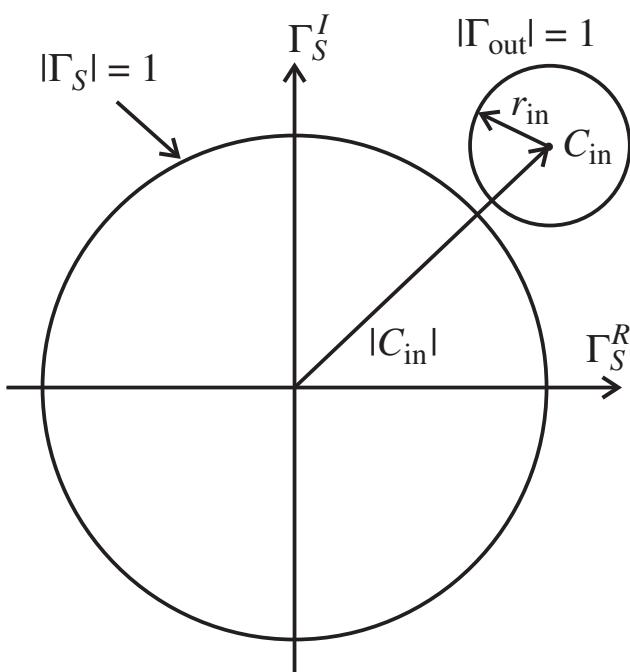

(a) $|\Gamma_{out}| = 1$ circle must reside outside

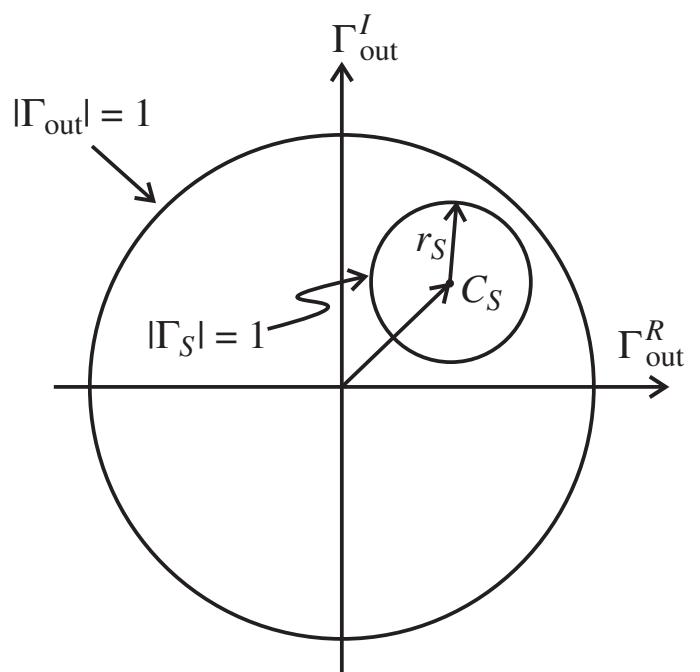

(b) $|\Gamma_S| = 1$ circle must reside inside

Figure 9-7 Unconditional stability in the Γ_S and Γ_{out} planes for $|S_{11}| < 1$.

Table 9-1 BFG505W S-parameters as functions of frequency

Frequency	S_{11}	S_{12}	S_{21}	S_{22}
500 MHz	$0.70\angle-57^\circ$	$0.04\angle47^\circ$	$10.5\angle136^\circ$	$0.79\angle-33^\circ$
750 MHz	$0.56\angle-78^\circ$	$0.05\angle33^\circ$	$8.6\angle122^\circ$	$0.66\angle-42^\circ$
1000 MHz	$0.46\angle-97^\circ$	$0.06\angle22^\circ$	$7.1\angle112^\circ$	$0.57\angle-48^\circ$
1250 MHz	$0.38\angle-115^\circ$	$0.06\angle14^\circ$	$6.0\angle104^\circ$	$0.50\angle-52^\circ$

Table 9-2 Stability parameters for BFG505W

f , MHz	k	$ \Delta $	C_{in}	r_{in}	C_{out}	r_{out}
500	0.41	0.69	$39.04 \angle 108^\circ$	38.62	$3.56 \angle 70^\circ$	3.03
750	0.60	0.56	$62.21 \angle 119^\circ$	61.60	$4.12 \angle 70^\circ$	3.44
1000	0.81	0.45	$206.23 \angle 131^\circ$	205.42	$4.39 \angle 69^\circ$	3.54
1250	1.02	0.37	$42.42 \angle 143^\circ$	41.40	$4.24 \angle 68^\circ$	3.22

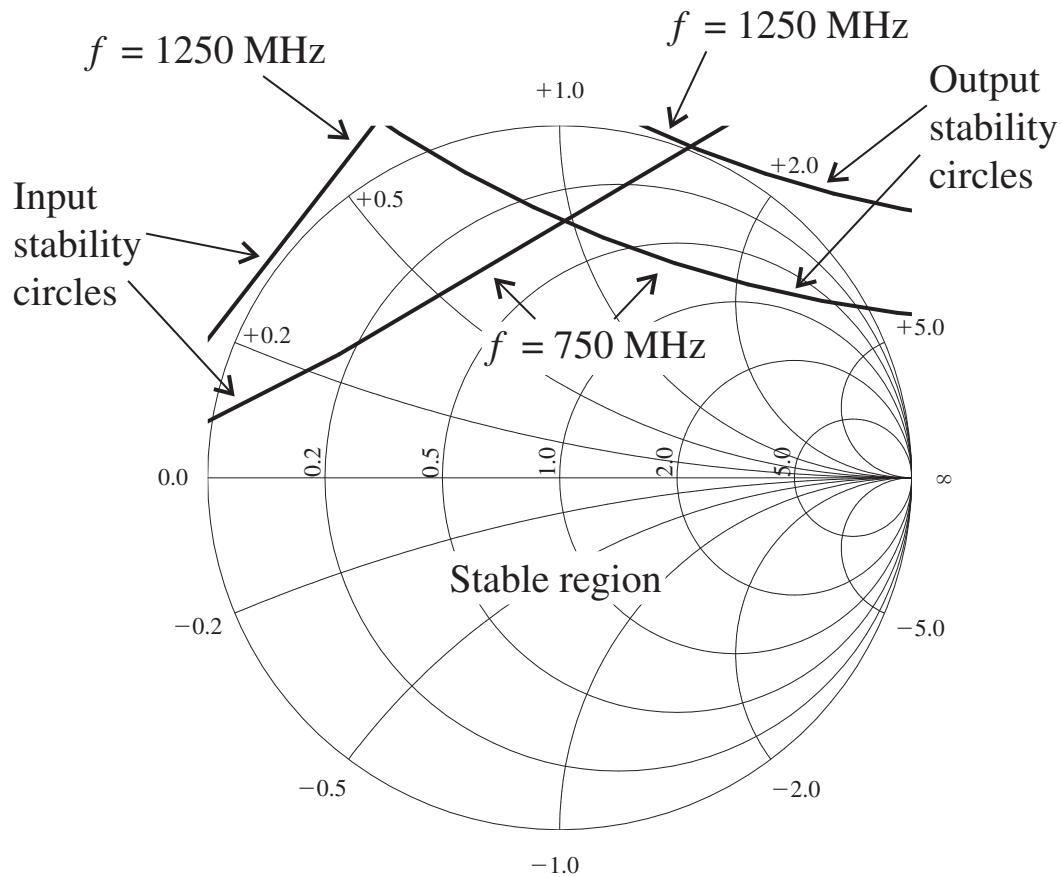


Figure 9-8 Input and output stability circles for BFG505W computed at $f = 750 \text{ MHz}$ and $f = 1.25 \text{ GHz}$.



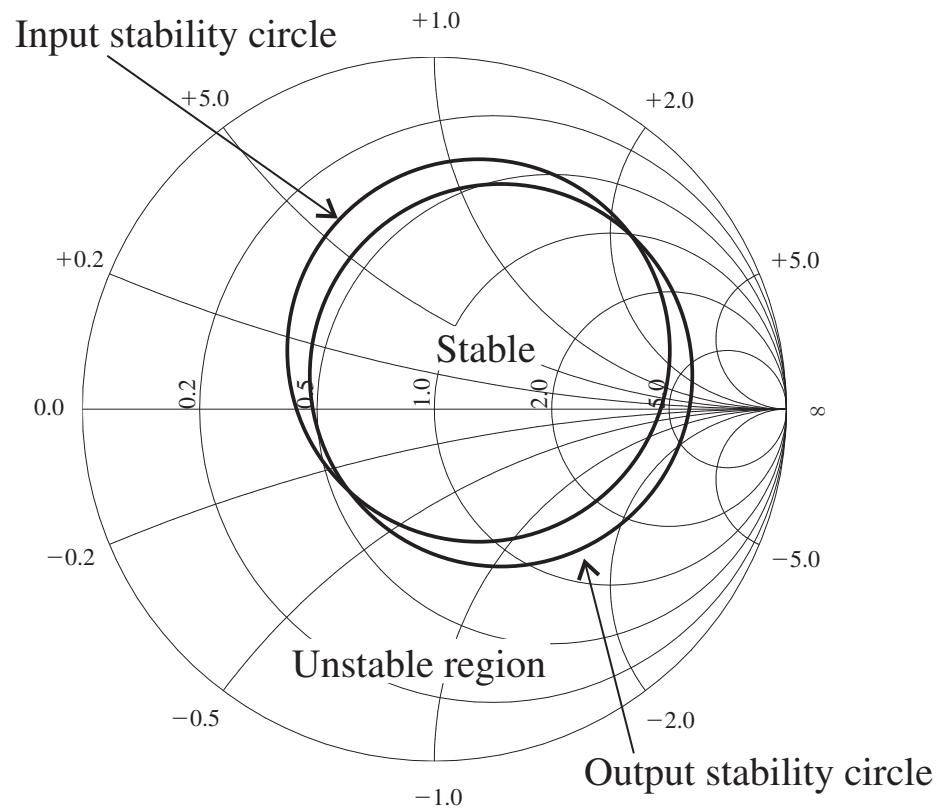


Figure 9-9 Stability circles for $k > 1$ and $|\Delta| > 1$.

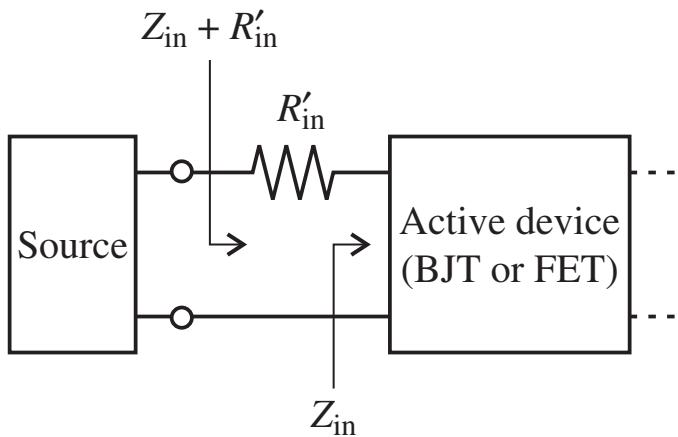


(a) Series resistance

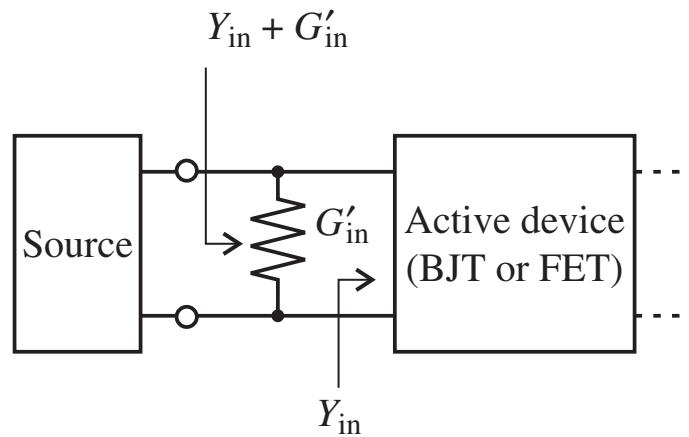


(b) Shunt conductance

Figure 9-10 Stabilization of input port through series resistance or shunt conductance.

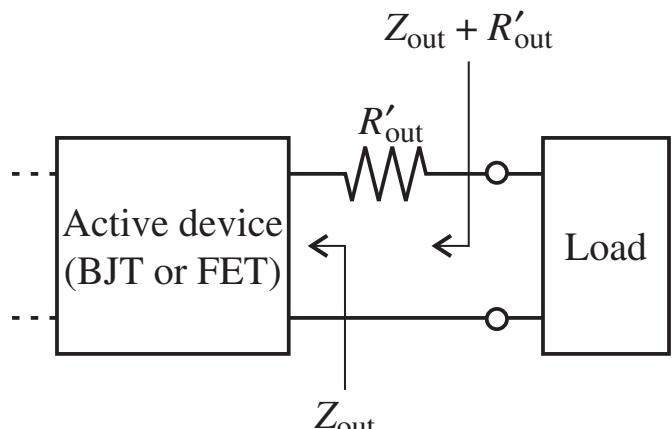

(a) Series resistance

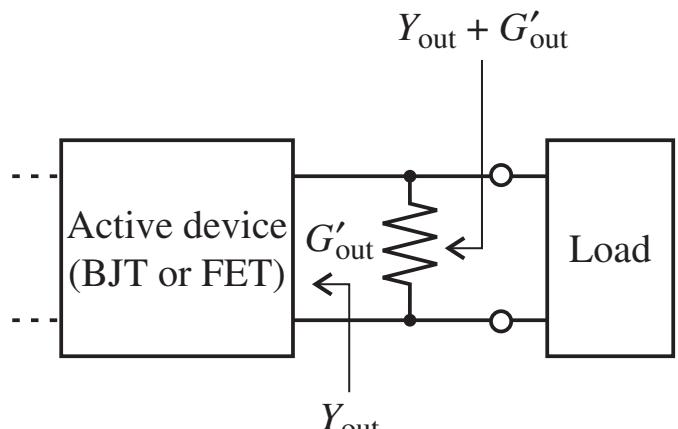

(b) Shunt conductance

Figure 9-11 Stabilization of output port through series resistance or shunt conductance.

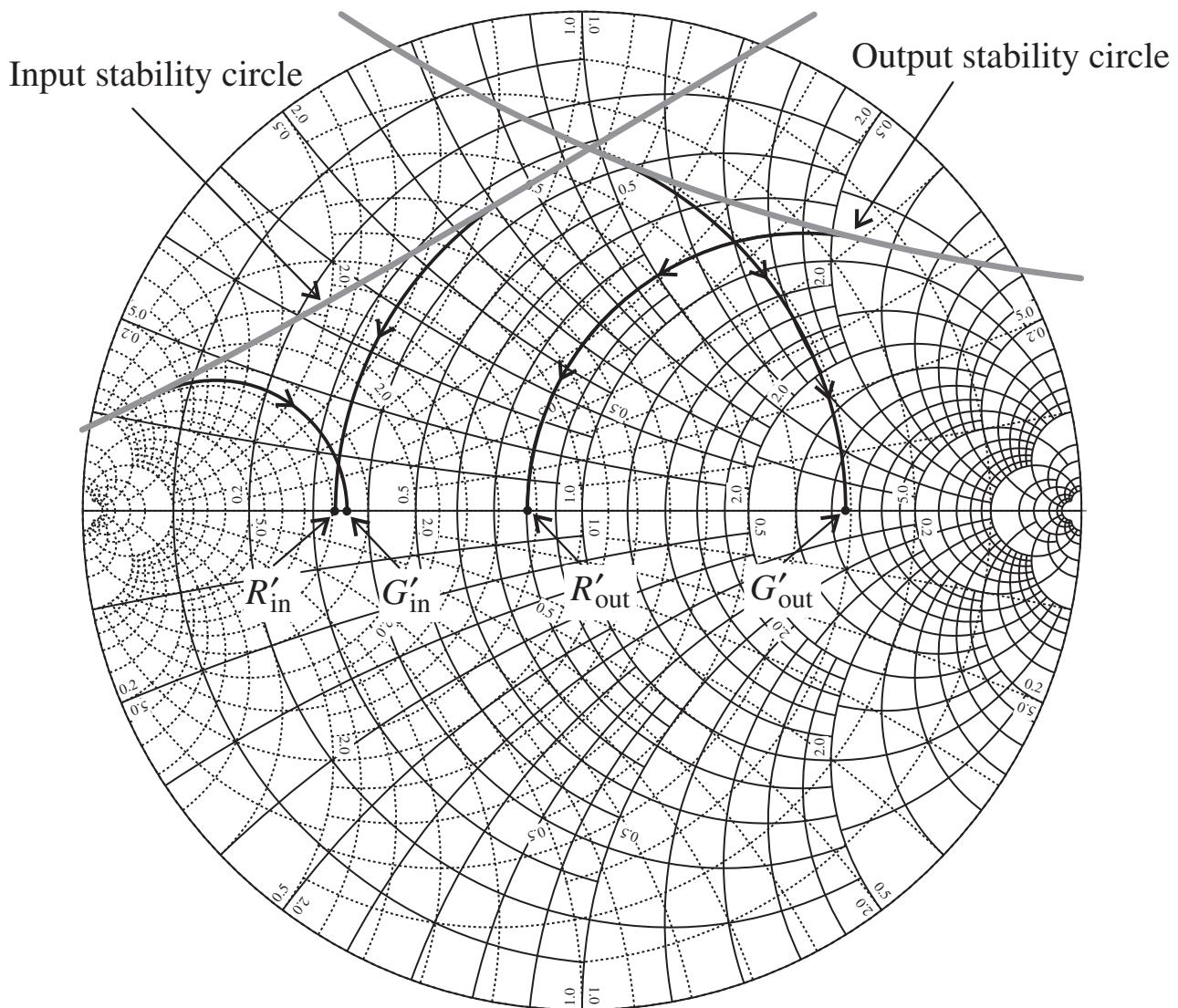


Figure 9-12 Input and output stability circles and circles for finding stabilizing series resistance and shunt conductances.

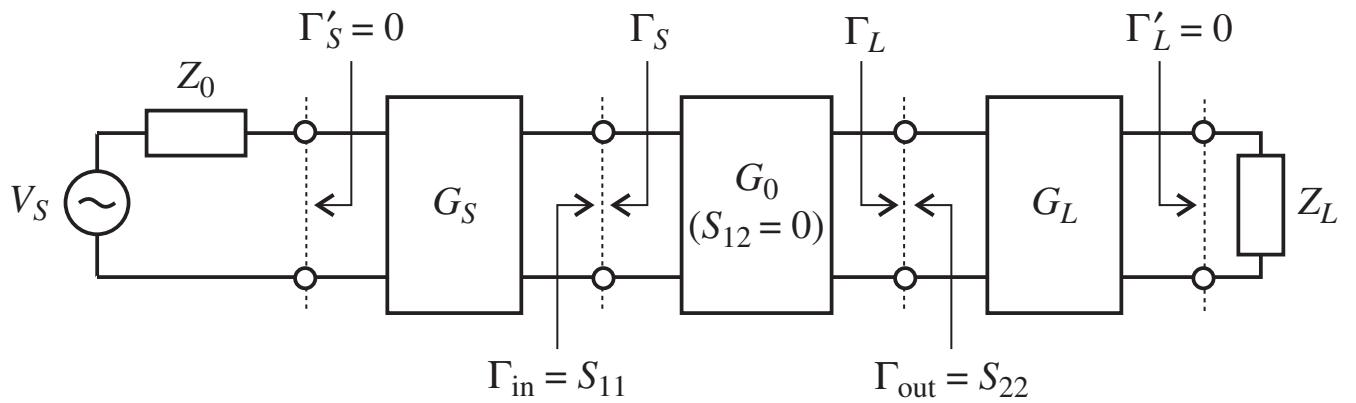


Figure 9-13 Unilateral power gain system arrangement.

Table 9-3 Parameters for constant source gain circles in Example 9-7

G_S	g_S	d_{g_S}	r_{g_S}
2.6 dB	0.93	$0.67 \angle -125^\circ$	0.14
2 dB	0.81	$0.62 \angle -125^\circ$	0.25
1 dB	0.64	$0.54 \angle -125^\circ$	0.37
0 dB	0.51	$0.47 \angle -125^\circ$	0.47
-1 dB	0.41	$0.40 \angle -125^\circ$	0.56

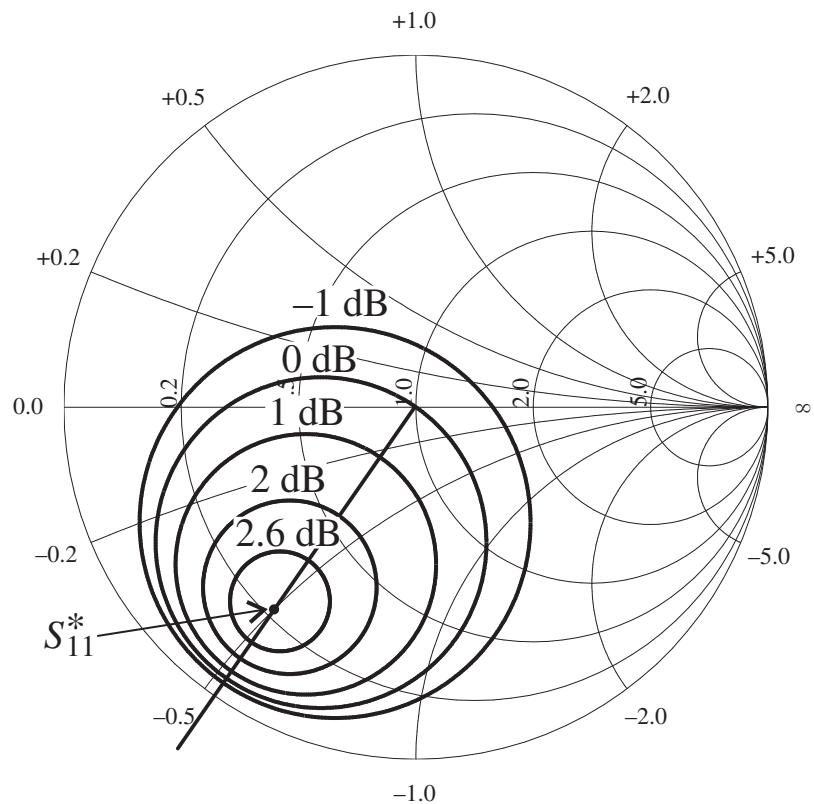


Figure 9-14 Constant source gain circles in the Smith Chart.

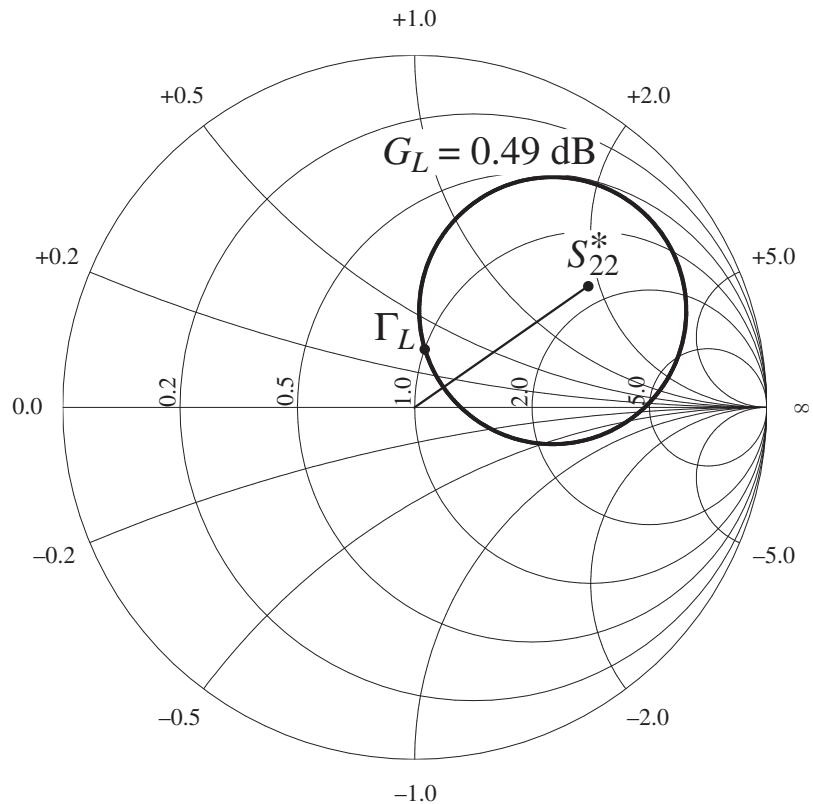


Figure 9-15 Constant load gain circle in the Smith Chart.

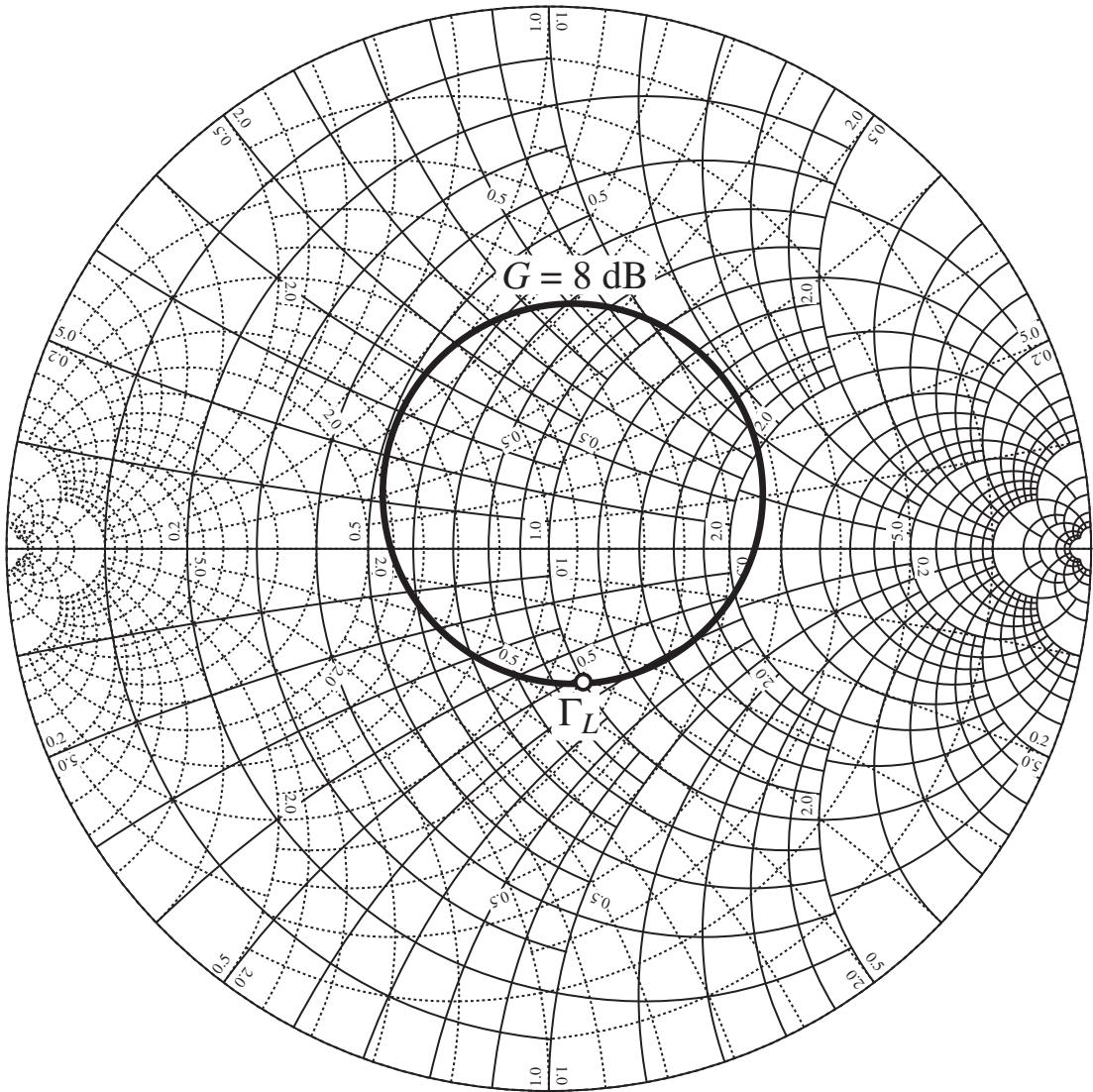


Figure 9-16 Constant operating power circle in the Γ_L -plane.

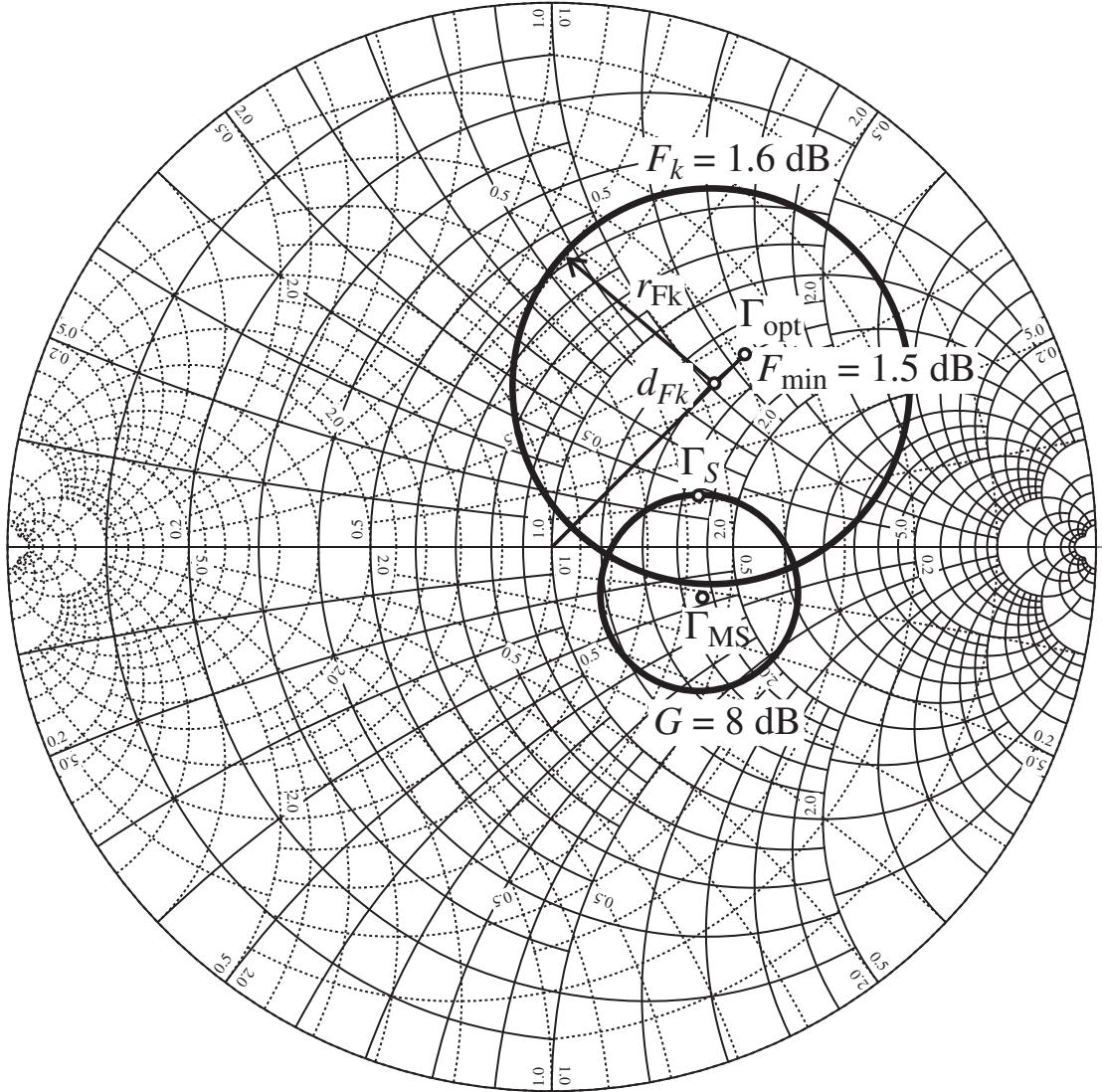


Figure 9-17 Constant noise figure circle and constant operating gain circle mapped into the Γ_S -plane.

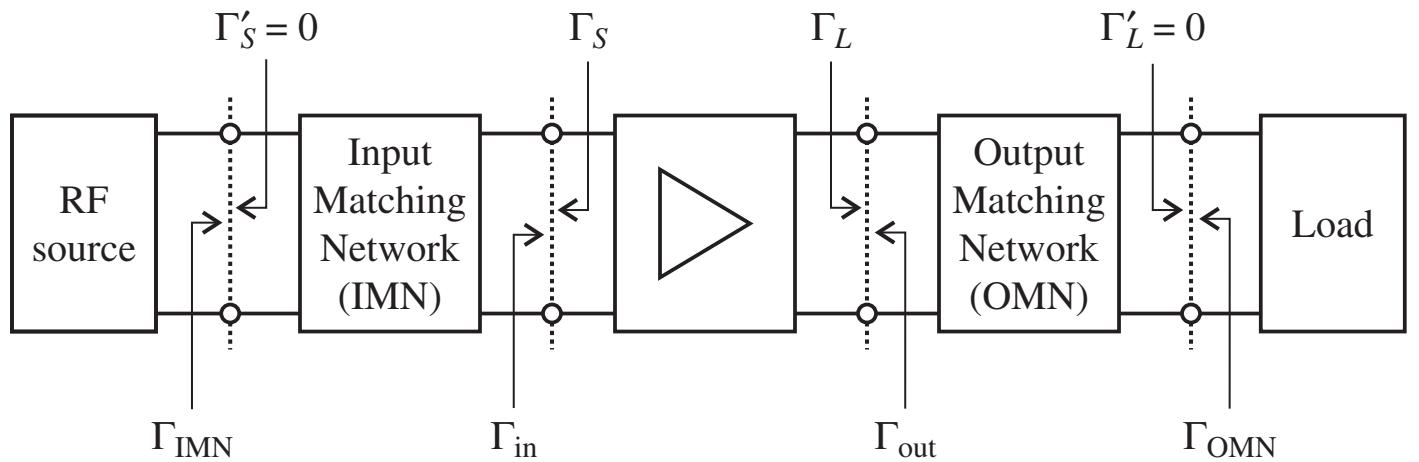


Figure 9-18 System configuration for input and output VSWR.

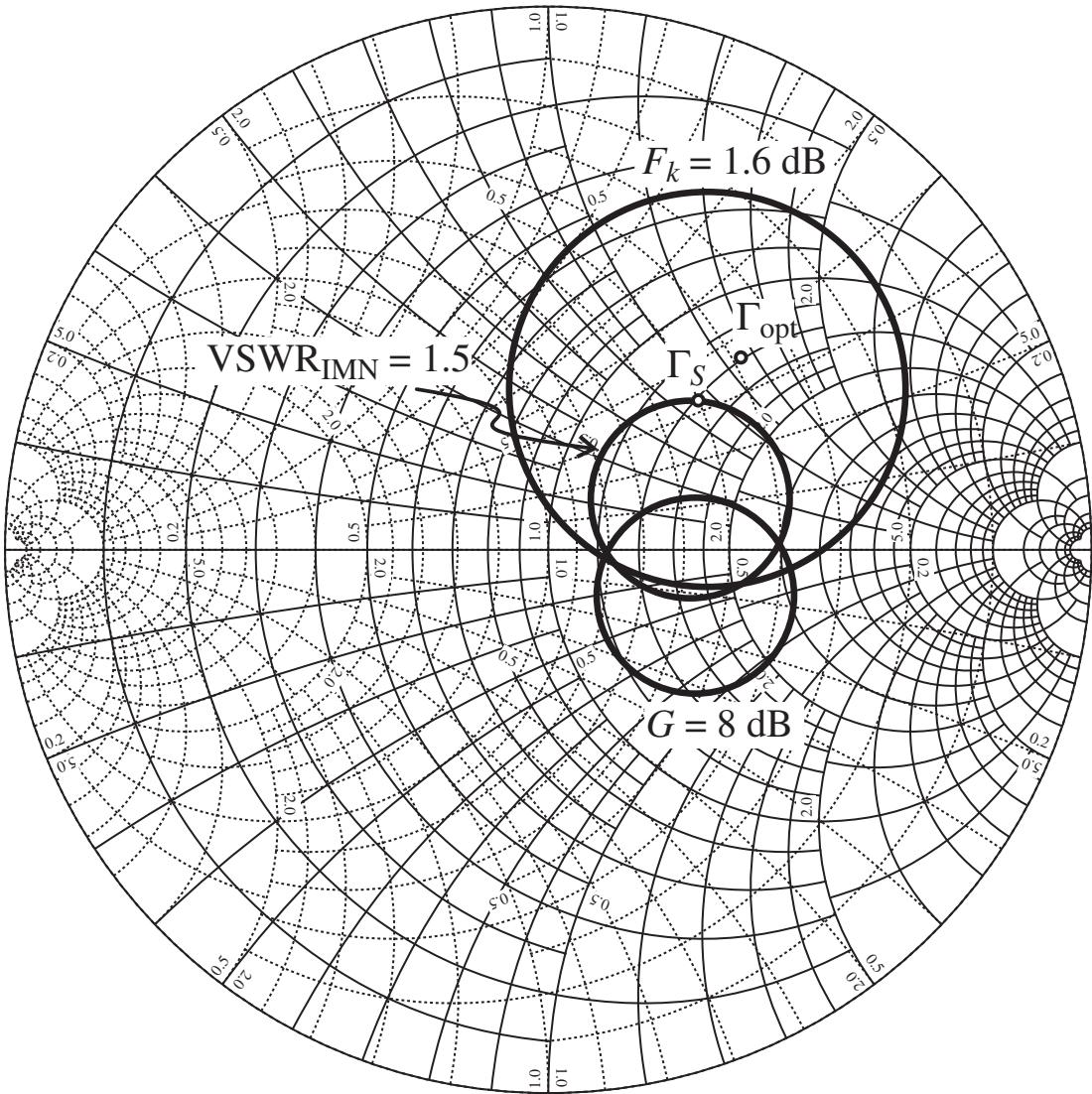


Figure 9-19 Constant operating power gain, noise figure, and input VSWR circle in Γ_S -plane.

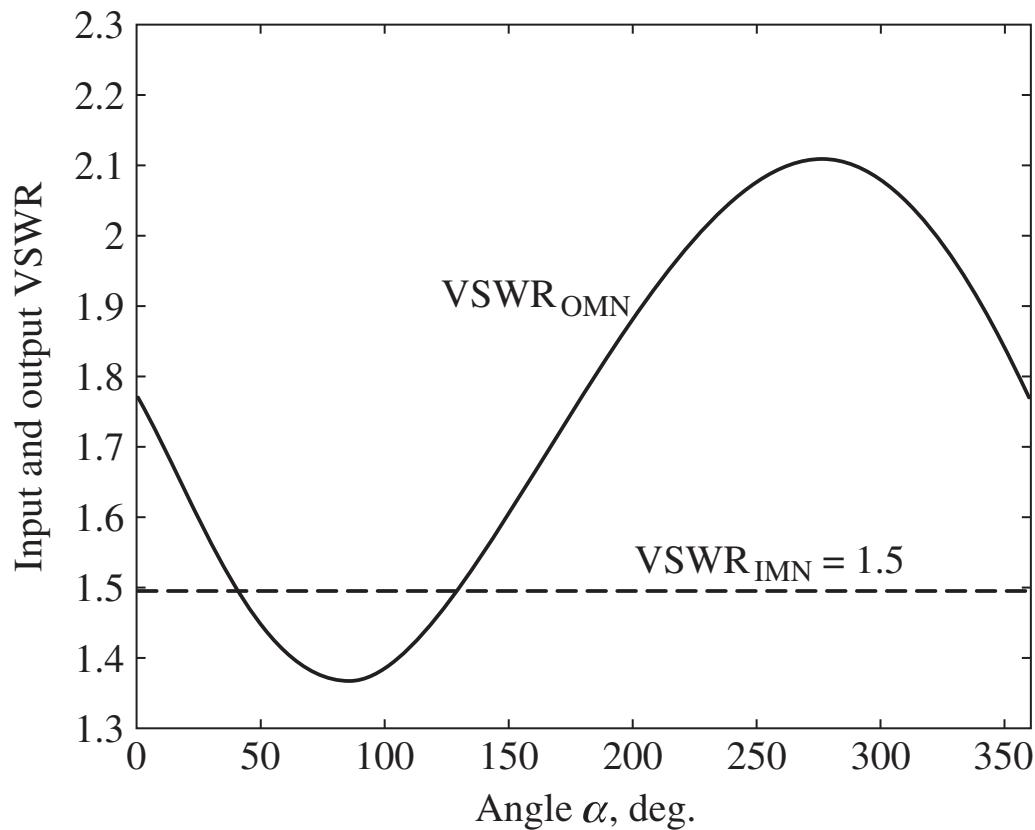


Figure 9-20 Input and output VSWR as a function of angle α .

Table 9-4 S-parameters of AT41410 BJT ($I_C = 10$ mA,
 $V_{CE} = 8$ V)

f , GHz	$ S_{21} $	S_{11}	S_{22}
2	3.72	$0.61 \angle 165^\circ$	$0.45 \angle -48^\circ$
3	2.56	$0.62 \angle 149^\circ$	$0.44 \angle -58^\circ$
4	1.96	$0.62 \angle 130^\circ$	$0.48 \angle -78^\circ$

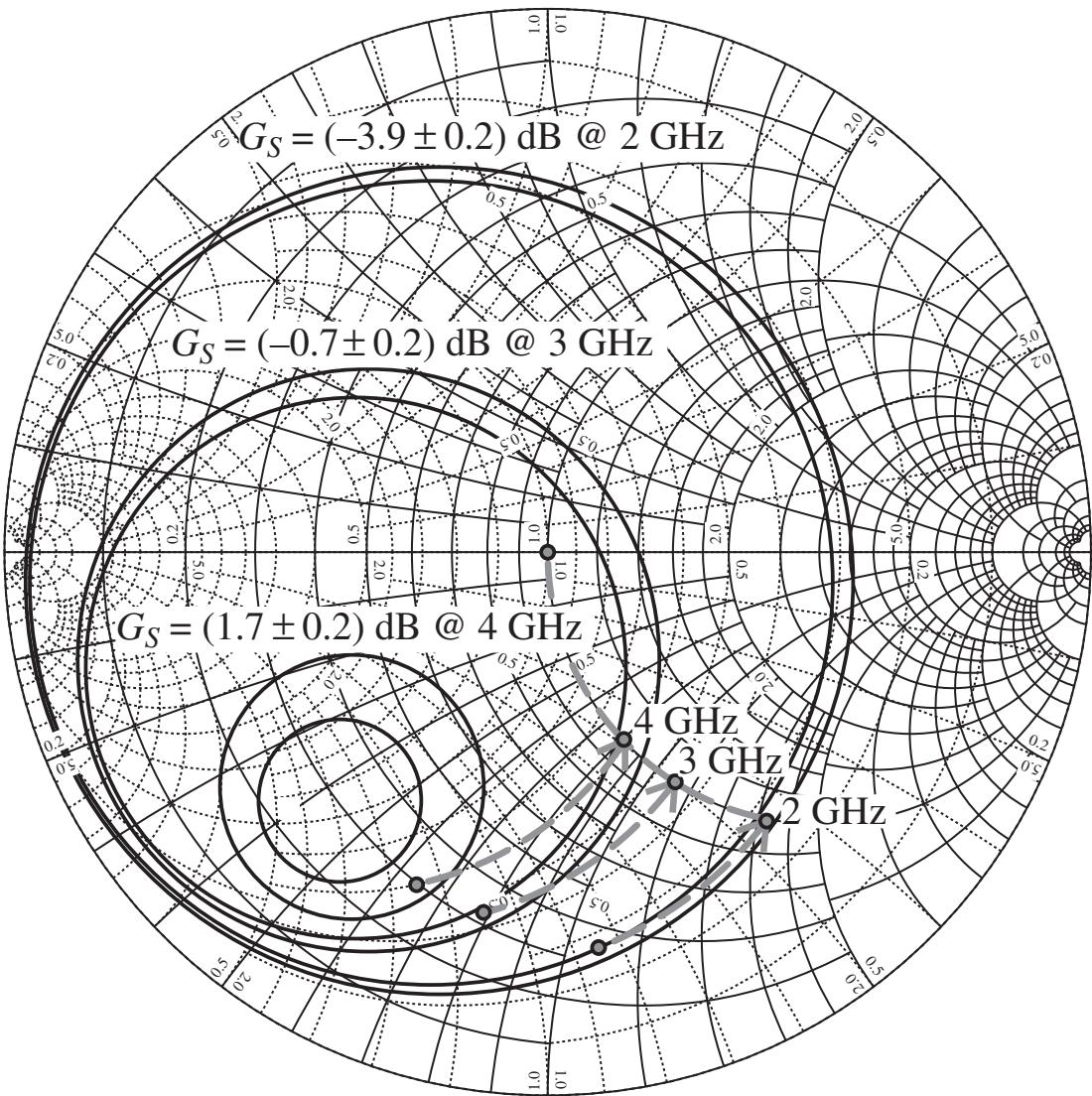


Figure 9-21 Smith Chart design of a broadband amplifier in Example 9-16.


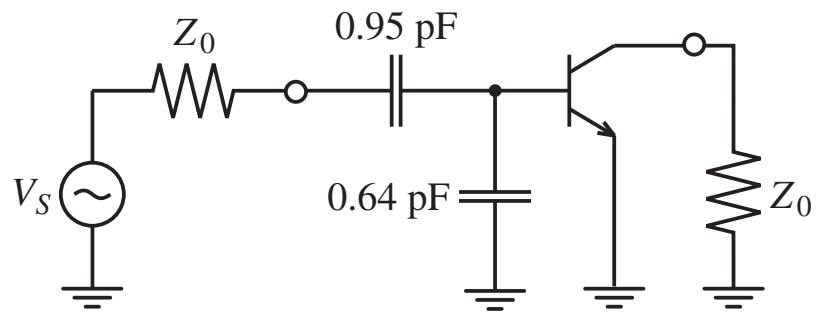



Figure 9-22 Broadband amplifier with 7.5 dB gain and ± 0.2 dB gain flatness over a frequency range from 2 to 4 GHz.

Table 9-5 Parameters of a broadband amplifier

f , GHz	Γ_S	G_T , dB	$VSWR_{IMN}$	$VSWR_{OMN}$
2	$0.74\angle-83^\circ$	7.65	13.1	2.6
3	$0.68\angle-101^\circ$	7.57	5.3	2.6
4	$0.66\angle-112^\circ$	7.43	2.0	2.8

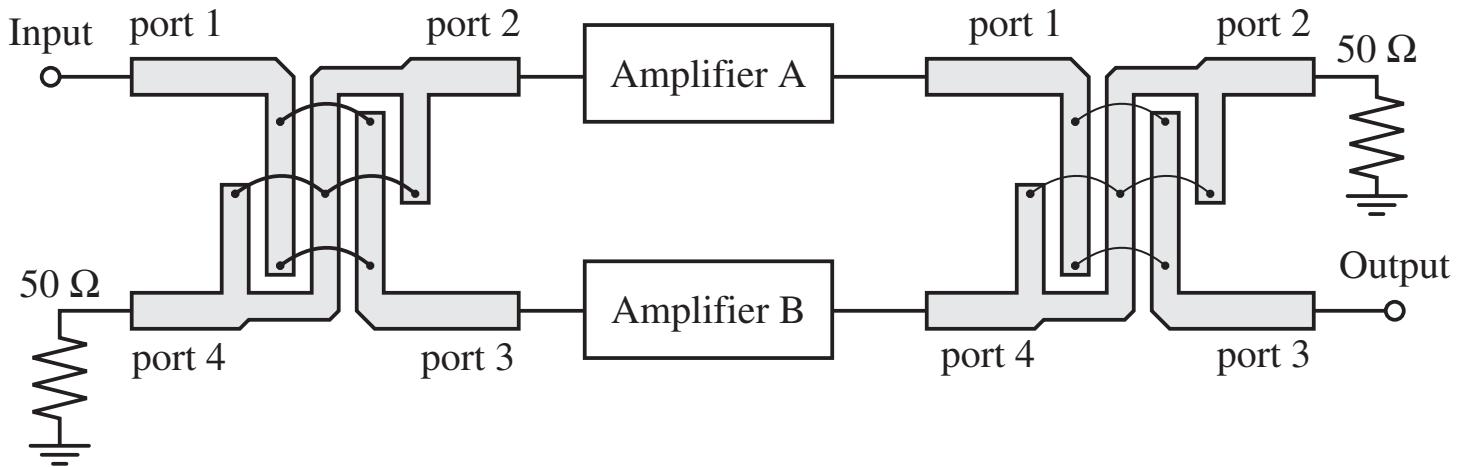


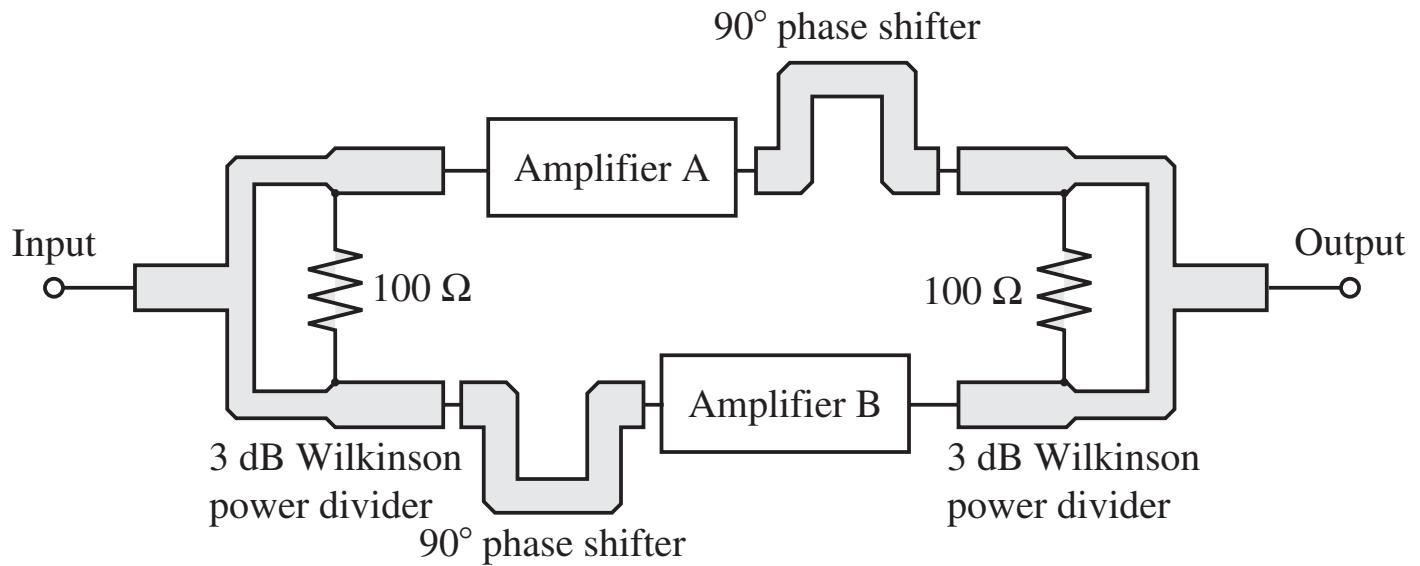(a) Balanced amplifier using 3 dB coupler




(b) Balanced amplifier using 3 dB Wilkinson power divider and combiner

Figure 9-23 Block diagram of a balanced broadband amplifier.

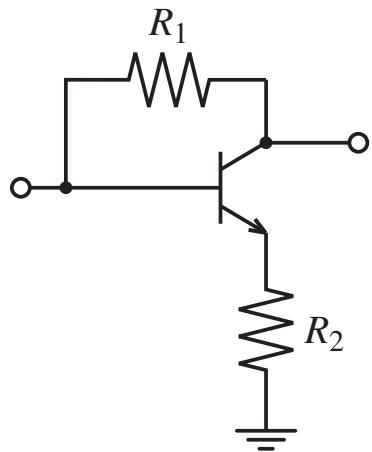

(a) Feedback in BJTs

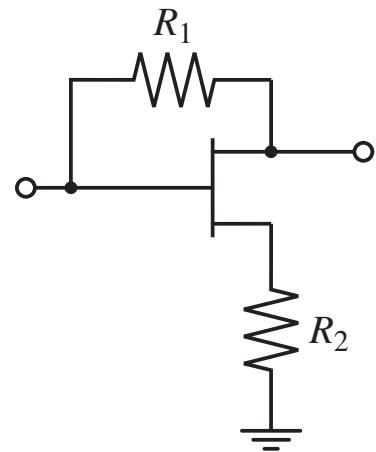

(b) Feedback in FETs

Figure 9-24 Negative resistive feedback circuits.

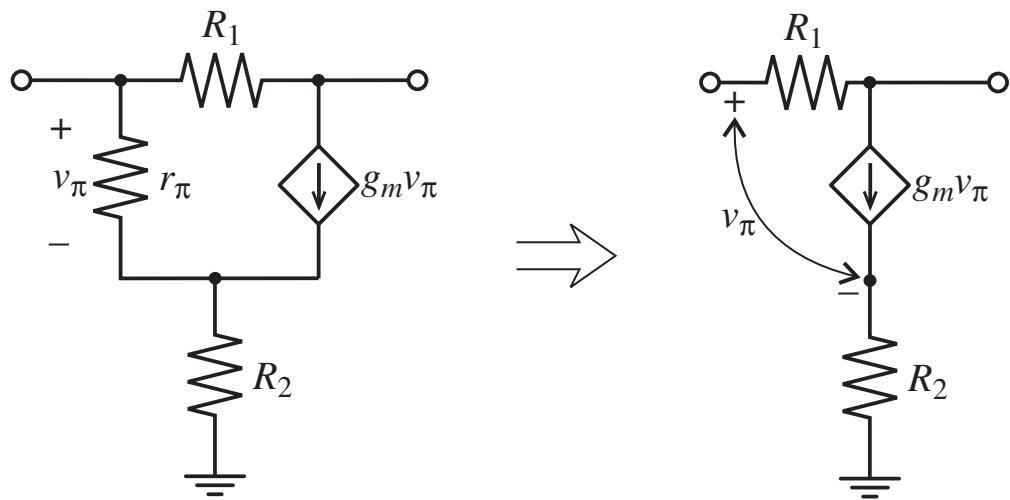


Figure 9-25 Low-frequency model of negative feedback circuit.

Table 9-6 S-parameters for the transistor in Example 9-17

f , MHz	$ S_{11} $	$\angle S_{11}$	$ S_{21} $	$\angle S_{21}$	$ S_{12} $	$\angle S_{12}$	$ S_{22} $	$\angle S_{22}$
10	0.877	-0.3°	7.035	179.6°	1×10^{-4}	66.8°	0.805	-0.1°
100	0.876	-2.4°	7.027	176.1°	7×10^{-4}	85.9°	0.805	-1.4°
250	0.870	-5.9°	6.983	170.2°	0.002	84.3°	0.803	-3.4°
500	0.850	-11.5°	6.834	160.6°	0.003	80.5°	0.797	-6.6°
750	0.820	-16.9°	6.607	151.4°	0.004	76.0°	0.789	-9.8°
1000	0.783	-21.7°	6.327	142.8°	0.005	68.2°	0.777	-12.7°
1500	0.700	-29.6°	5.711	127.2°	0.007	74.1°	0.755	-18.1°
2000	0.619	-35.7°	5.119	113.8°	0.007	74.1°	0.735	-23.0°

Table 9-7 Insertion gain of the feedback amplifier

f , MHz	$ S_{21} ^2$, dB		
	$R_1 = 208 \Omega$, $R_2 = 4.1 \Omega$	$R_1 = 276 \Omega$, $R_2 = 1.4 \Omega$	$R_1 = 276 \Omega$, $R_2 = 1.4 \Omega$, $L_1 = 4.5 \text{ nH}$
10	7.50	10.01	10.01
100	7.50	10.01	10.01
250	7.50	10.00	10.01
500	7.50	9.97	10.00
750	7.50	9.93	10.00
1000	7.50	9.88	10.00
1500	7.51	9.75	9.99
2000	7.54	9.59	9.99

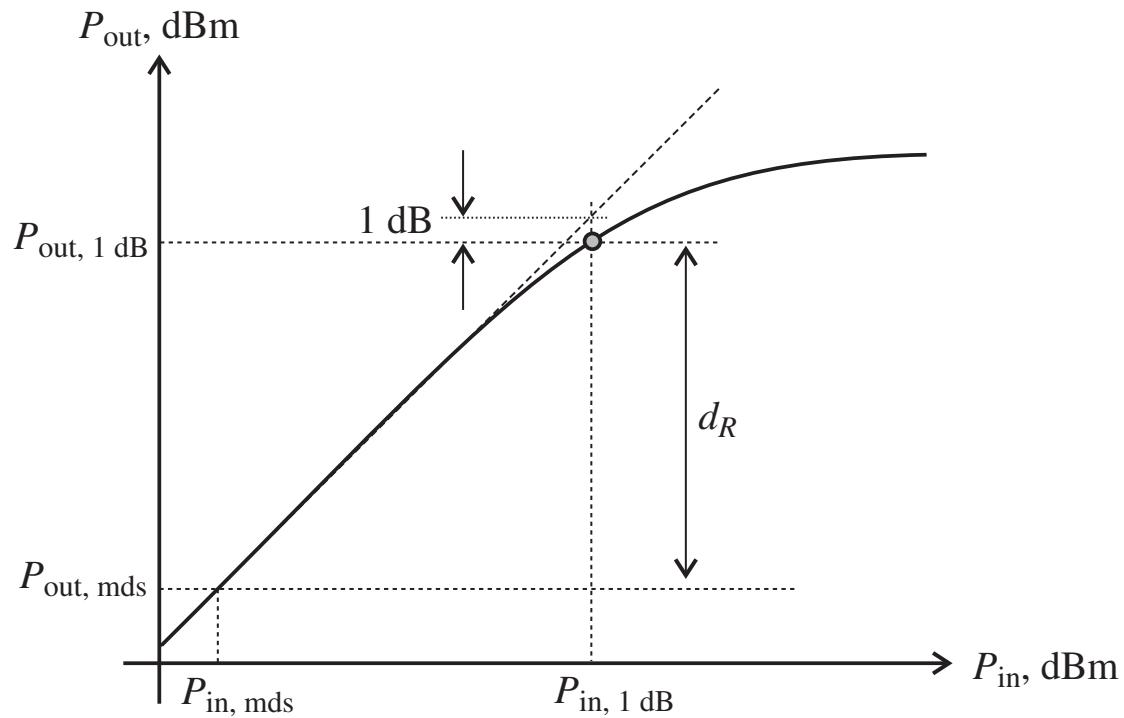


Figure 9-26 Output power of the amplifier as a function of input power.

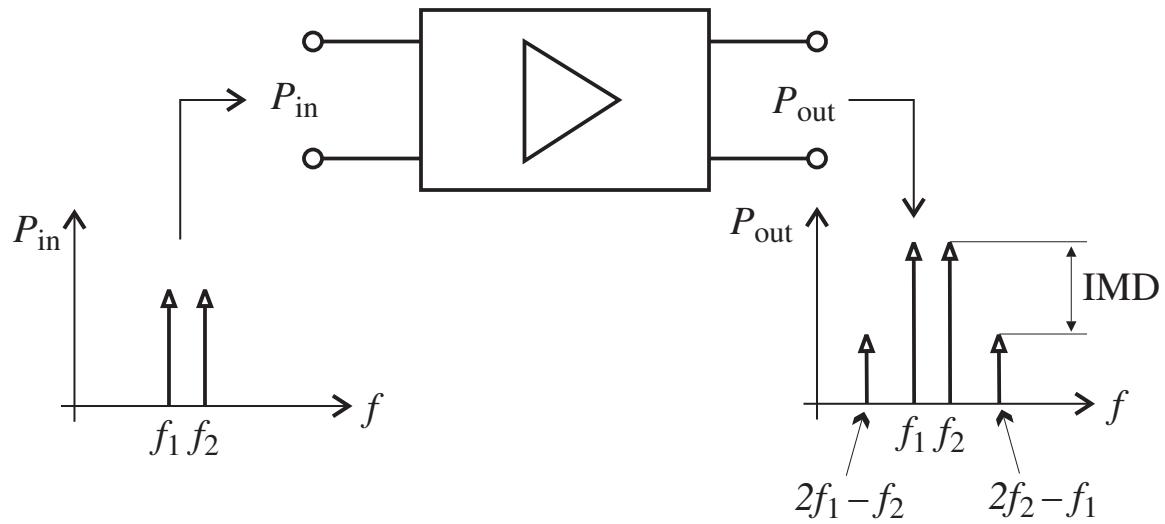


Figure 9-27 Observing the intermodulation distortion of an amplifier.

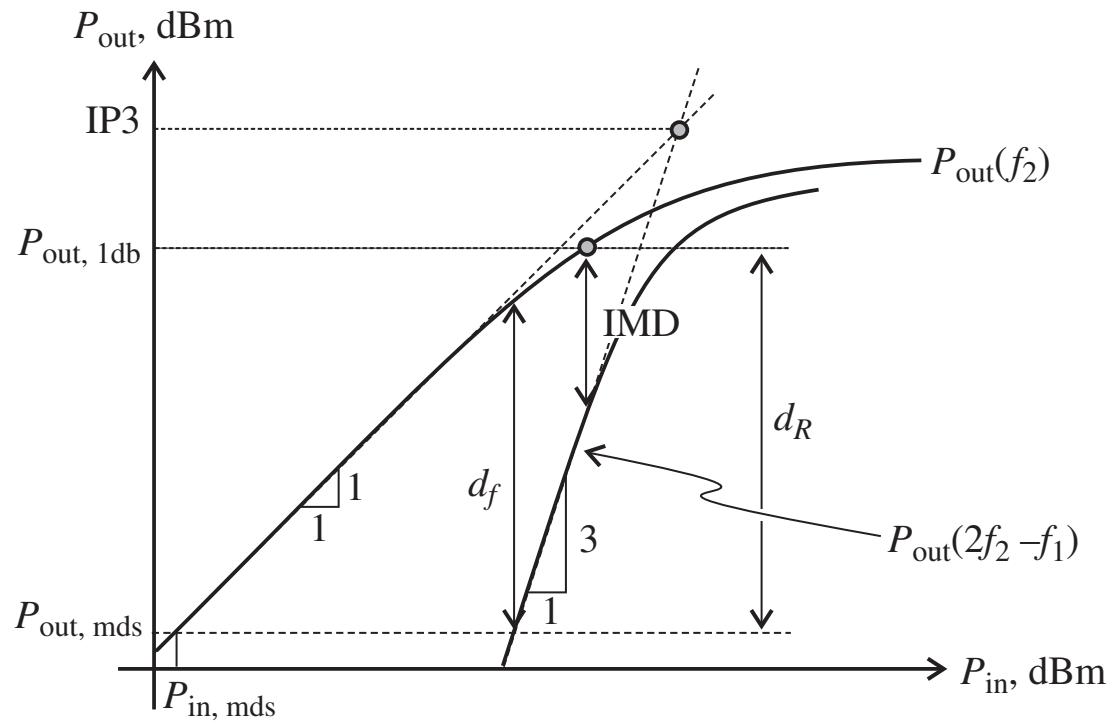


Figure 9-28 Recording of IMD based on input-output power relation.

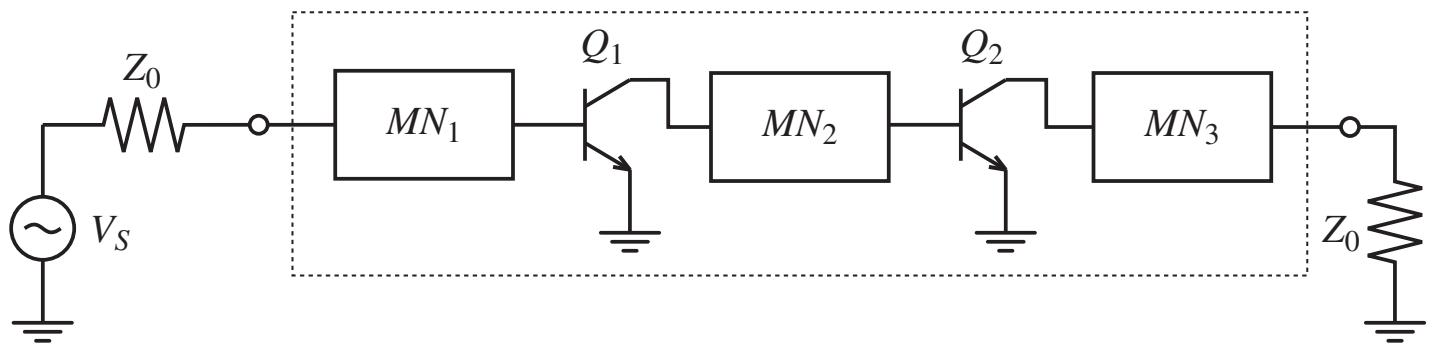


Figure 9-29 Dual-stage transistor amplifier.

Table 9-8 Transistor characteristics for Example 9-18

Transistor	$F[\text{dB}]$	$G_{\max}[\text{dB}]$	$P_{\text{out}, 1\text{dB}}[\text{dBm}]$	$\text{IP3}[\text{dBm}]$
BFG505	1.9	10	4	10
BFG520	1.9	9	17	26
BFG540	2	7	21	34



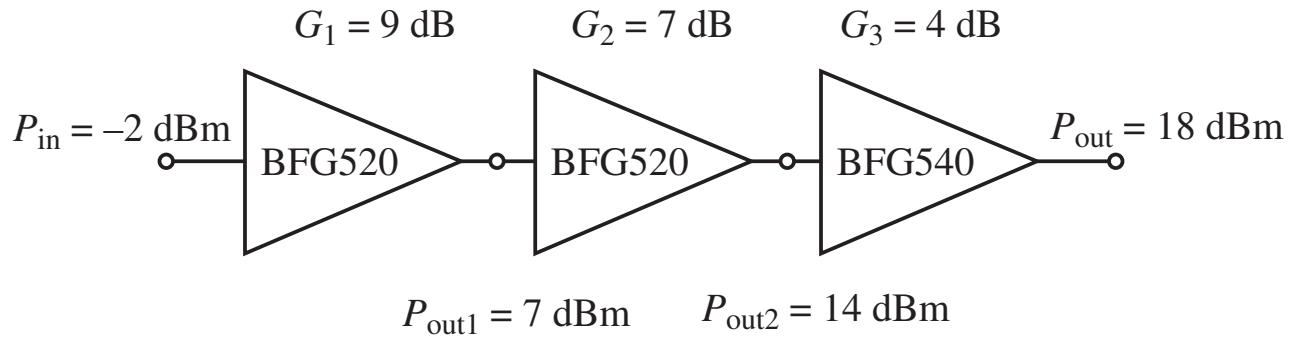


Figure 9-30 Block diagram of a three-stage amplifier.

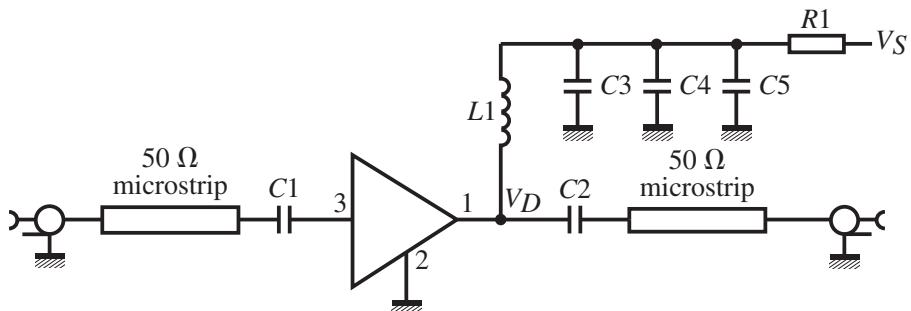


(a)

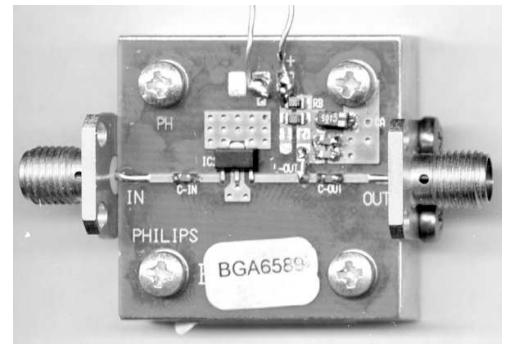


(b)


Figure 9-31 The MMIC amplifier schematic (courtesy of NXP) installed in a typical application circuit (a), and the corresponding layout (b).

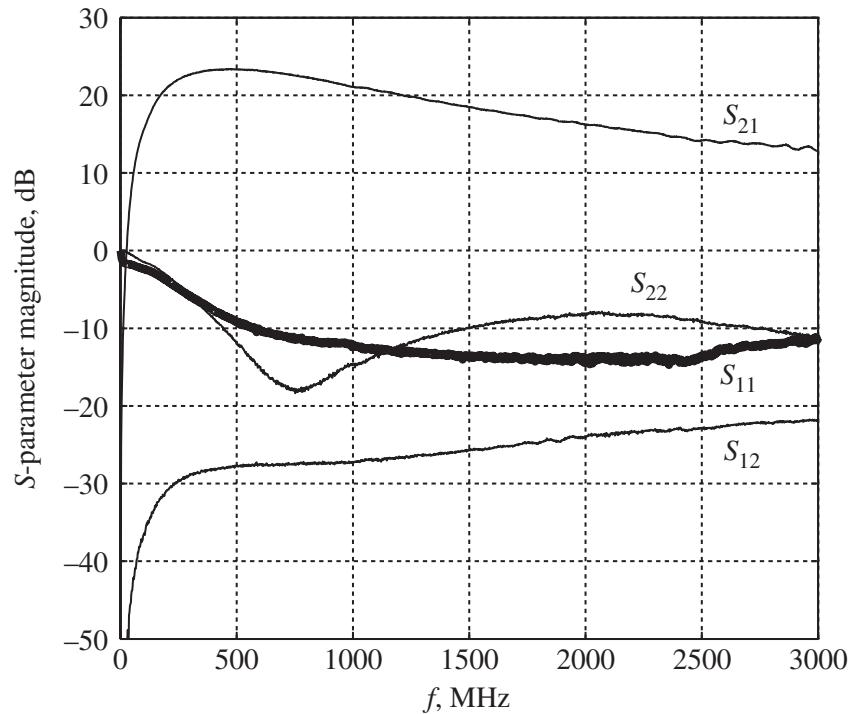

(a)

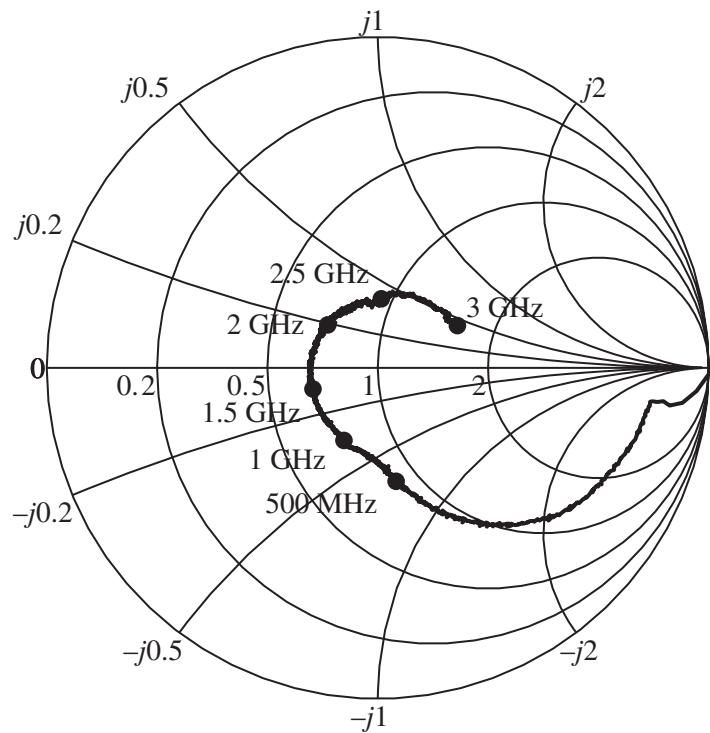


(b)

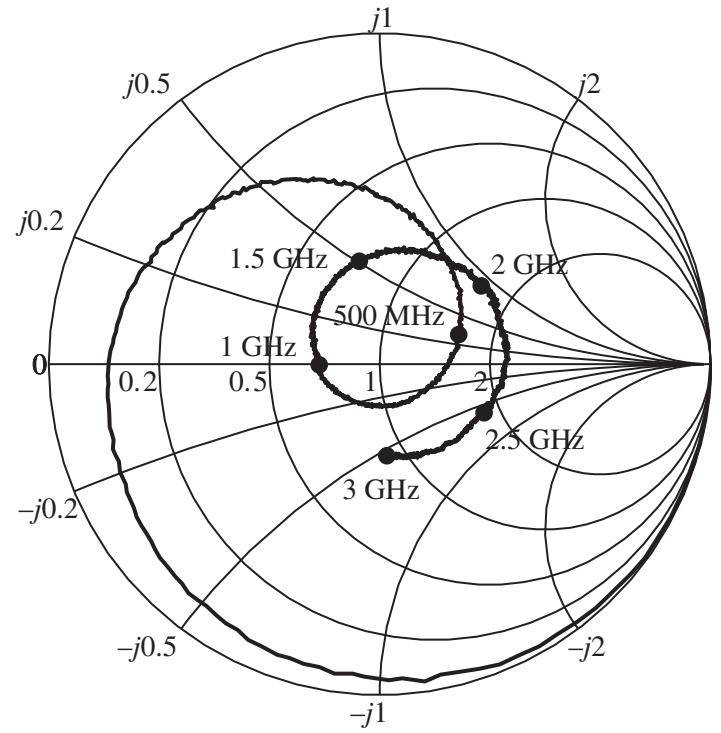


(c)

Figure 9-32 Measured MMIC amplifier S-parameters: (a) magnitude, (b) S₁₁ values displayed in Smith Chart, and (c) S₂₂ values displayed in Smith Chart.

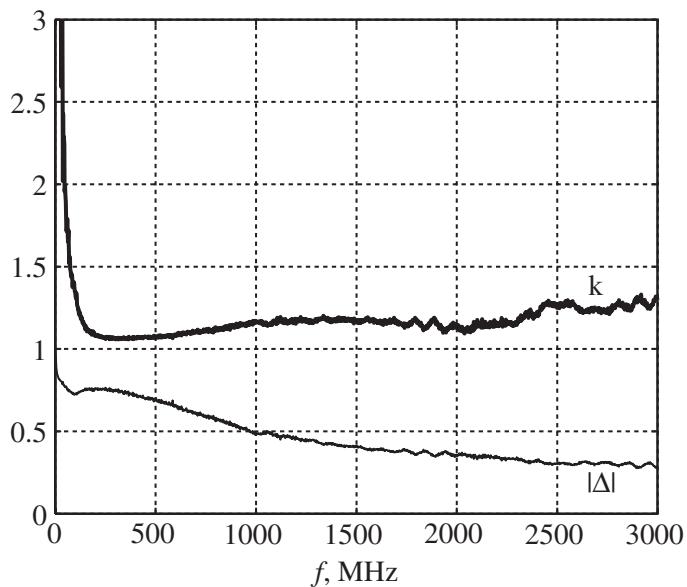

(a)

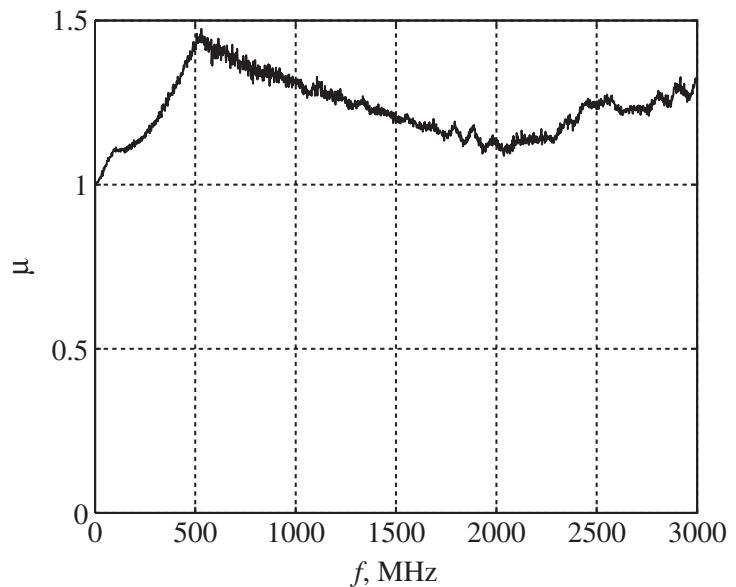

(b)

Figure 9-33 Stability factors determined from the S-parameter measurements:
(a) Rollett stability factor, (b) μ -test.

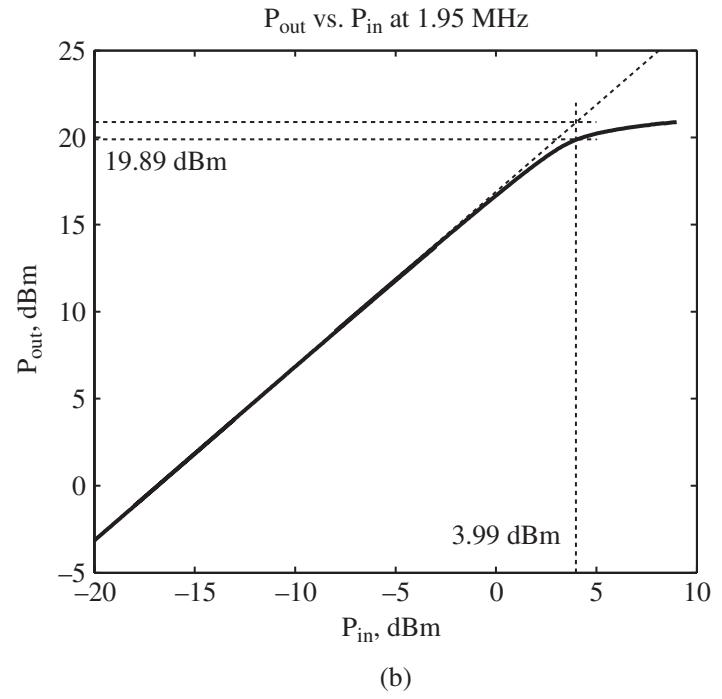
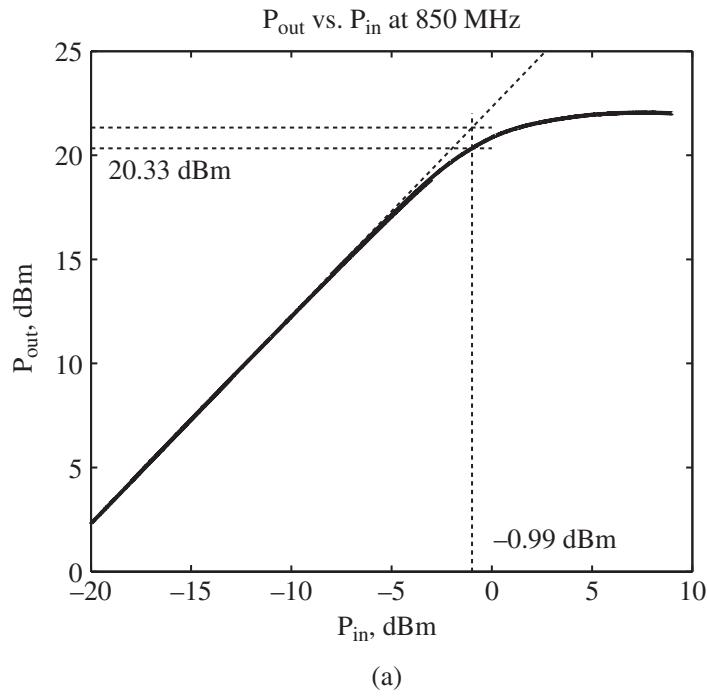


Figure 9-34 Gain compression observed in power sweeps at (a) 850 MHz and (b) 1.95 GHz.

Table 9-9 Comparison between the datasheet and network analyzer measurements

Parameter	850 MHz		1.95 GHz	
	Datasheet	Measured	Datasheet	Measured
Insertion power gain ($ S_{21} ^2$)	22 dB	22.1 dB	17 dB	16.6 dB
Input return loss	9 dB	11.7 dB	11 dB	13.8 dB
Output return loss	10 dB	17.2 dB	13 dB	8.4 dB
Stability factor k	1.1	1.13	1.1	1.15
Output power at 1 dB gain compression	21 dBm	20.3 dBm	20 dBm	19.9 dBm